

Unit 6.

Transconductances of MOSFET and BJT

Voltage gain of amplifier stages

MOSFET voltage amplifier stage

MOSFET transconductance


Small-signal equivalents:
 π -model vs T-model

Load line

Voltage gain of a common-source
amplifier stage with resistive load

BJT transconductance

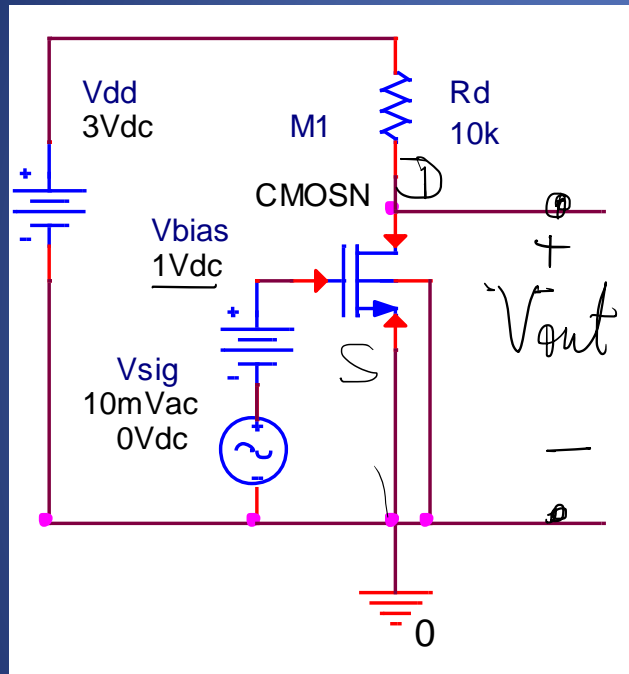Example: Voltage Amplifier with Common Source



$$A_v = \frac{V_{out}}{V_{in}} \text{ --- ?}$$

$$W = 10 \mu m \quad L = 0.5 \mu m$$

$$K_n' = 200 \frac{\mu A}{V^2} \quad V_{bias} = 1V$$

$$1) V_{ov} = V_{bias} - V_{th}$$


$$1 - 0.7 = 0.3V$$

$$2) I_{D_{SAT}} = \frac{1}{2} K_n' \frac{W}{L} V_{ov}^2 = \frac{200}{2} \cdot 20 \cdot 0.09 = 180 \mu A$$


One can estimate the drain current with this expression only in the saturation region:

it is required to have $V_{DS} > V_{ov} = 0.3V$. Indeed, $V_{DS} = V_{dd} - I_D \cdot R_d = 3 - 0.18mA \cdot 10k = 1.2V > \frac{0.3V}{2}$

Common-Source Gain Stage

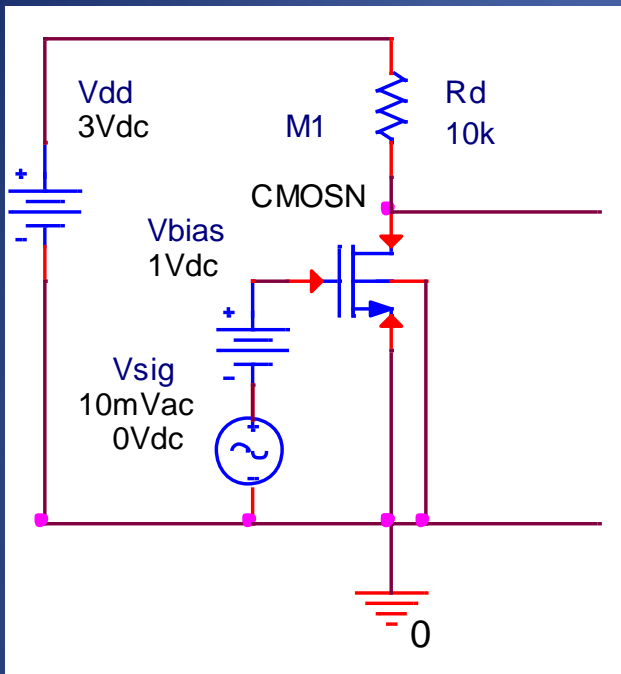

TRANSFER CHARACTERISTIC: I_D VS V_{GS}

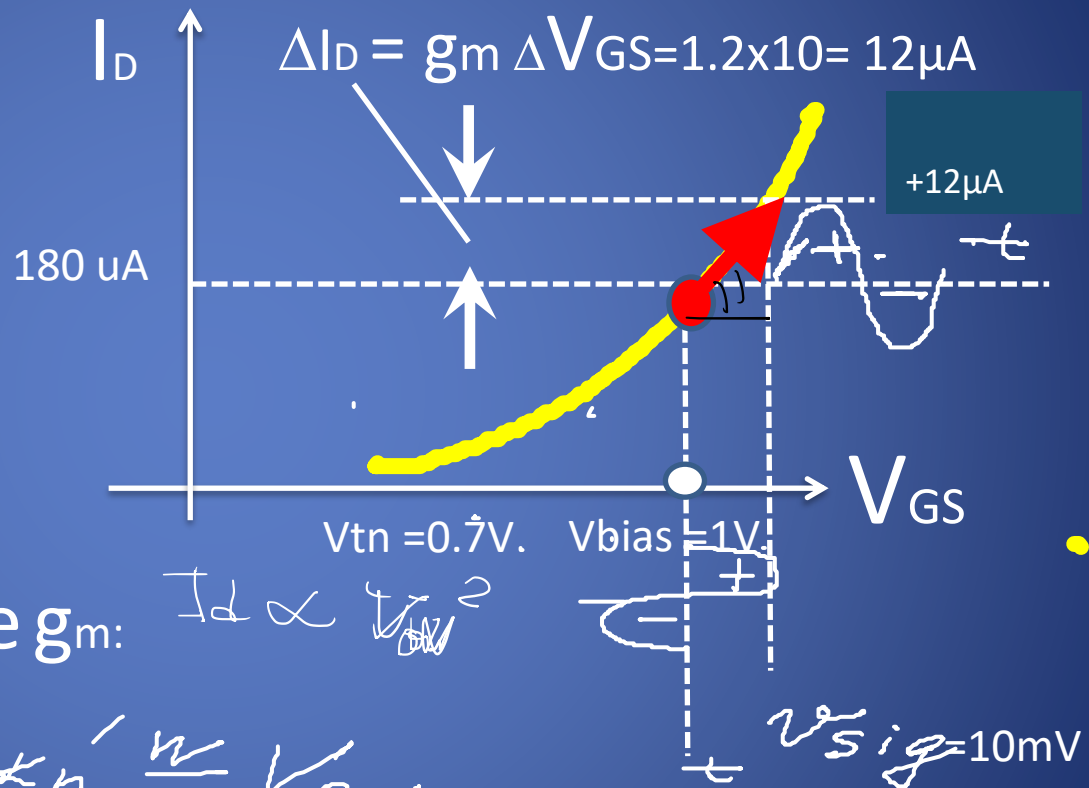

Transconductance g_m :

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}} = k_n' \frac{W}{L} V_{ov}$$

$$g_m = 200 \frac{\mu A}{V^2} \cdot 20 \cdot 0.3 = 1.2 \frac{mA}{V}$$

Estimation of the MOSFET transconductance from operating point (DC) parameters

$$g_m = K_n' \frac{W}{L} \cdot V_{ov}$$

$$I_D = \frac{1}{2} \left(K_n' \frac{W}{L} \cdot V_{ov} \cdot V_{ov} \right)$$


$$I_D = \frac{1}{2} g_m V_{ov}$$

$$g_m = \frac{2 I_D}{V_{ov}}$$

$$g_m = \frac{2 \cdot 0.18 \text{ mA}}{0.3 \text{ V}} = \frac{0.36}{0.3} = 1.2 \frac{\text{mA}}{\text{V}}$$




MOSFET output characteristics

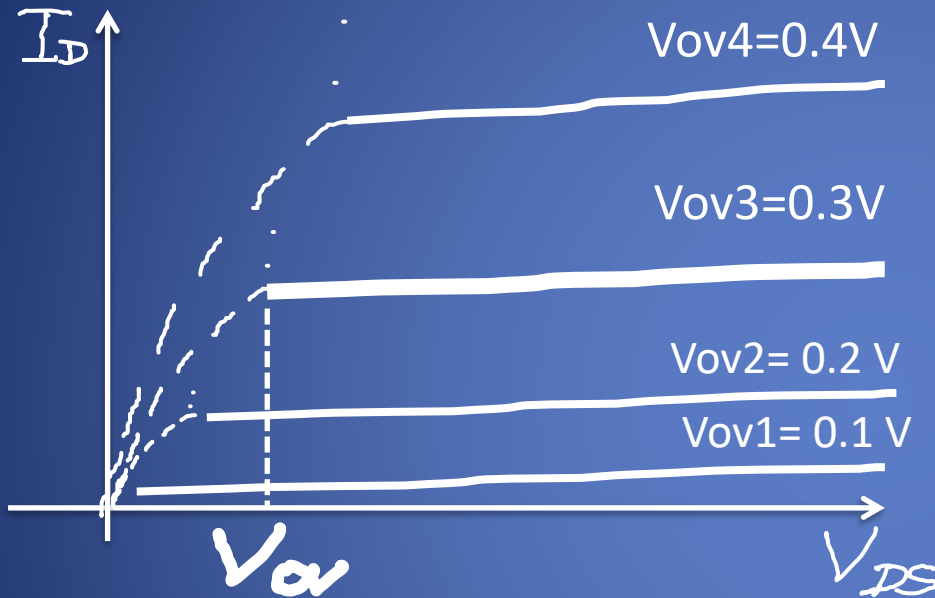


Small-signal model of the MOSFET:

π -model
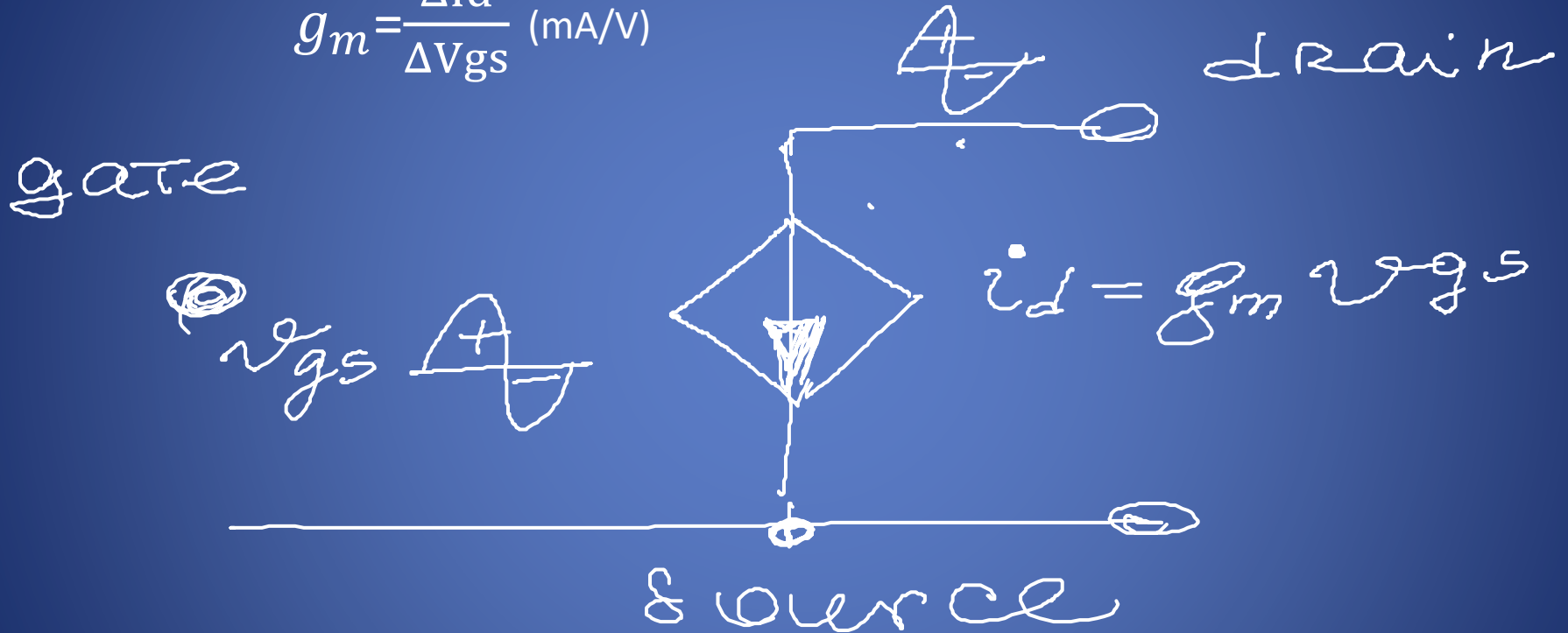
$$g_m = \frac{\Delta I_d}{\Delta V_{gs}} \text{ (mA/V)}$$





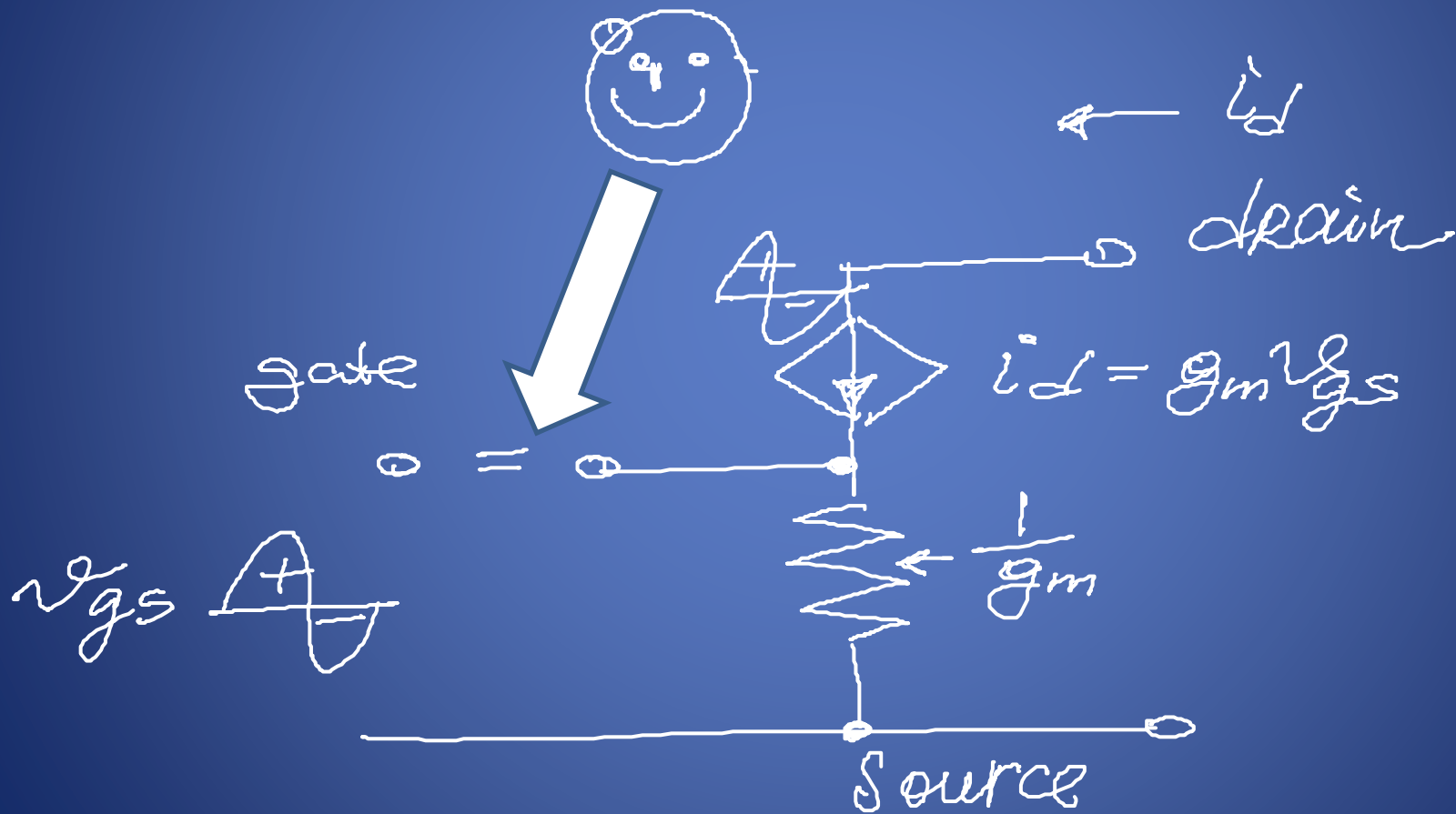Alternative small-signal model of the MOSFET: T-model



Load Line equation: $V_{DD} = V_{DS} + I_D R_D$

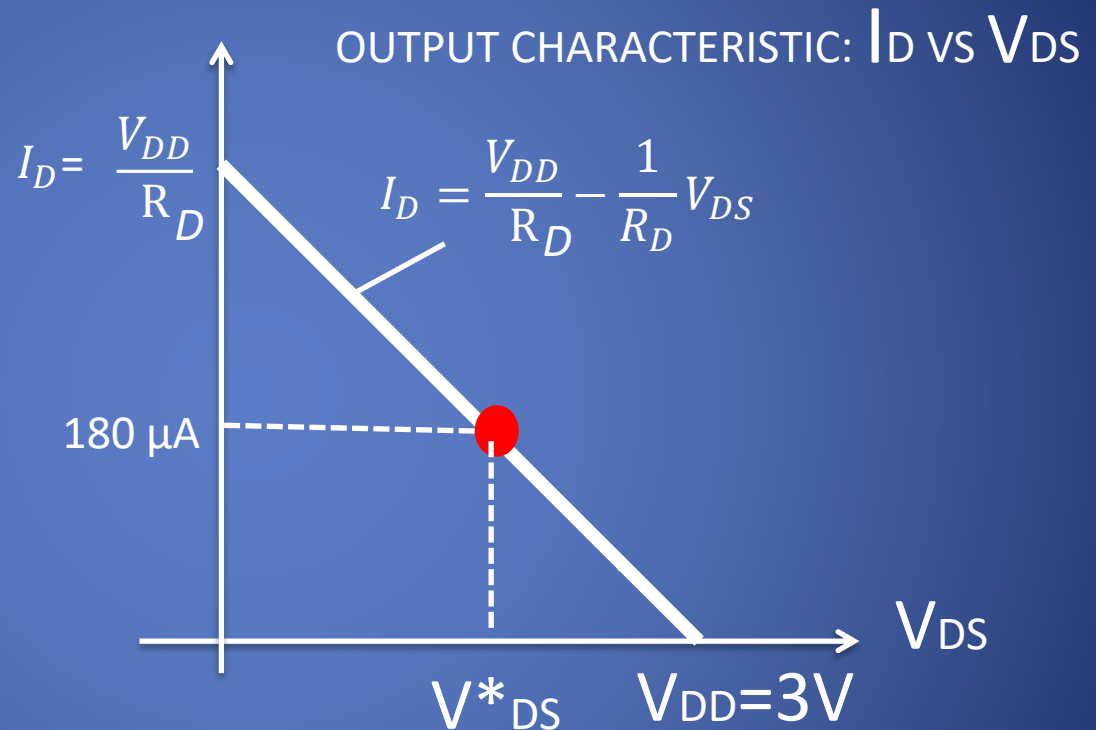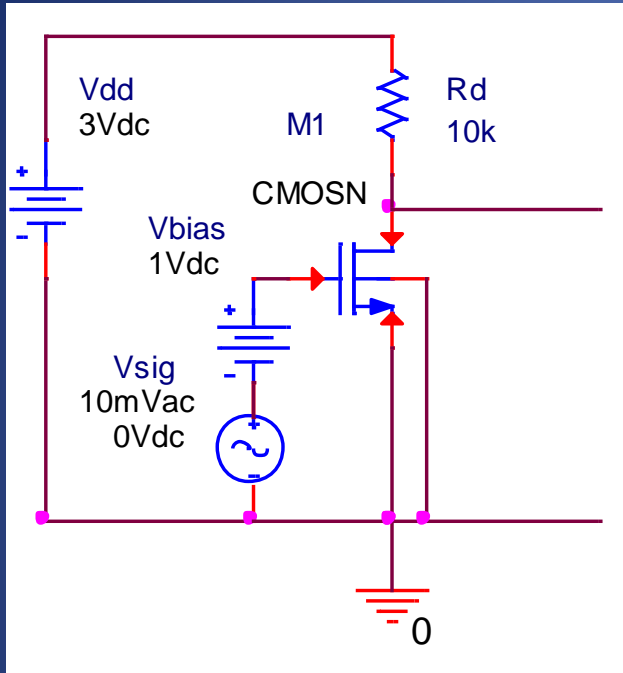R_D converts change of I_D into change of V_{DS} :




$$V_{DS}^* = V_{DD} - I_D R_D = 3 - 0.18 \text{ mA} \times 10\text{k} = 1.2 \text{ V} > V_{OV} = 0.3 \text{ V}$$


Indeed, MOSFET operates in the saturation mode and use of the square law for estimation of the drain current was adequate

Load Line equation: $V_{DD} = V_{DS} + I_D R_D$

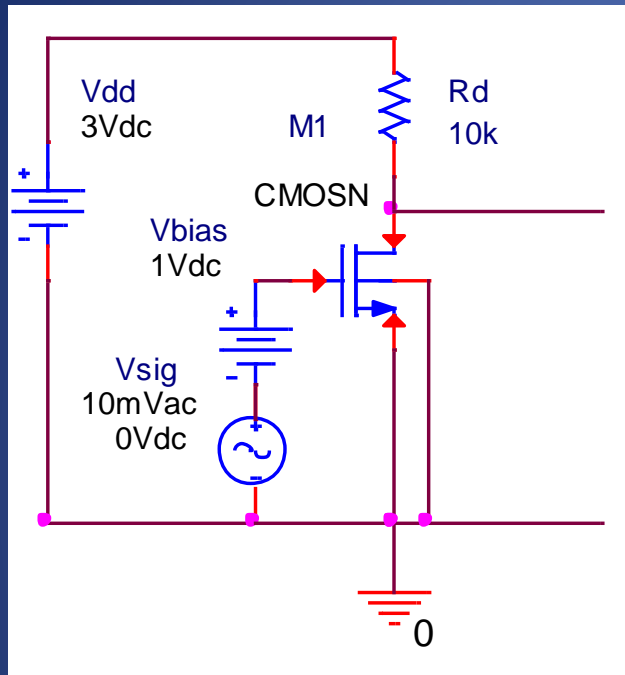R_D converts change of I_D into change of V_{DS} :



OUTPUT CHARACTERISTIC: I_D vs V_{DS}

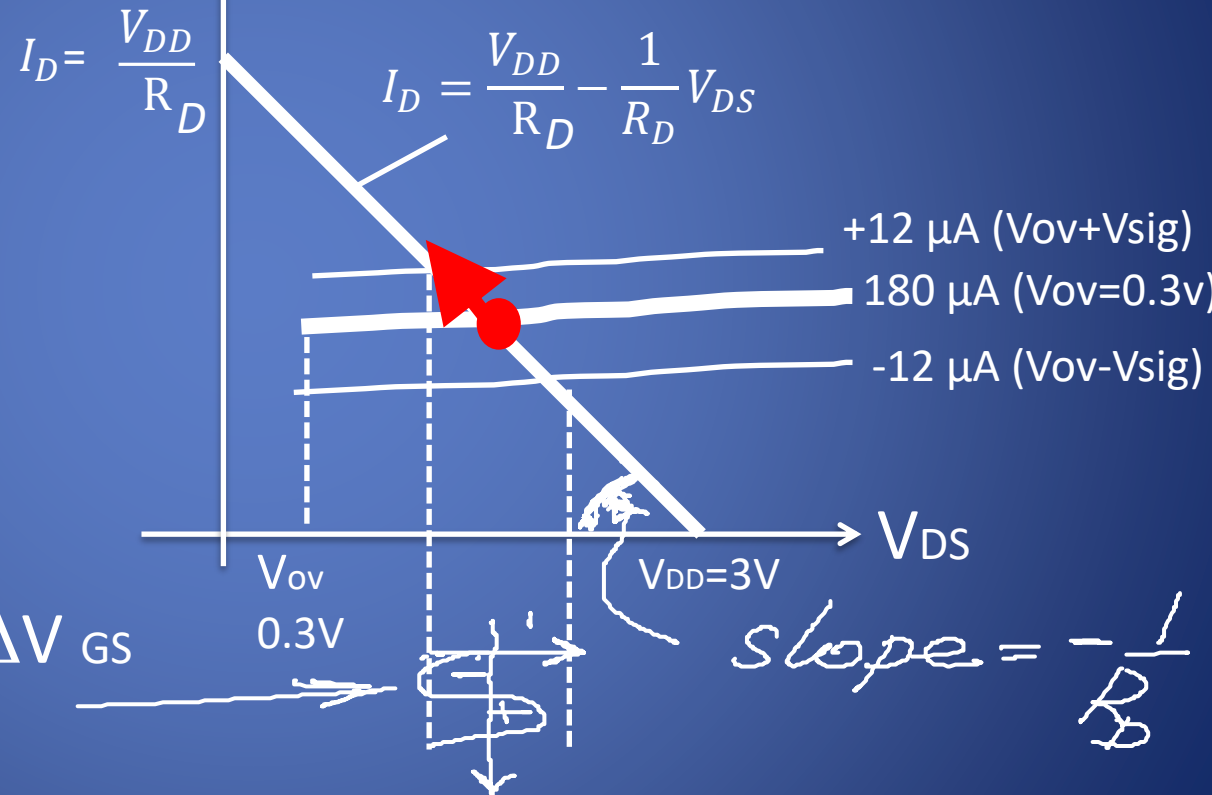


$$\Delta V_{DS} = -\Delta I_D R_D = g_m R_D \Delta V_{GS}$$

$$|A_v| = g_m R_D = 1.2 \frac{mA}{V} \cdot 10 k\Omega = 12 \text{ times only}$$

Small signal model of the MOSFET amplifier stage with Common Source configuration

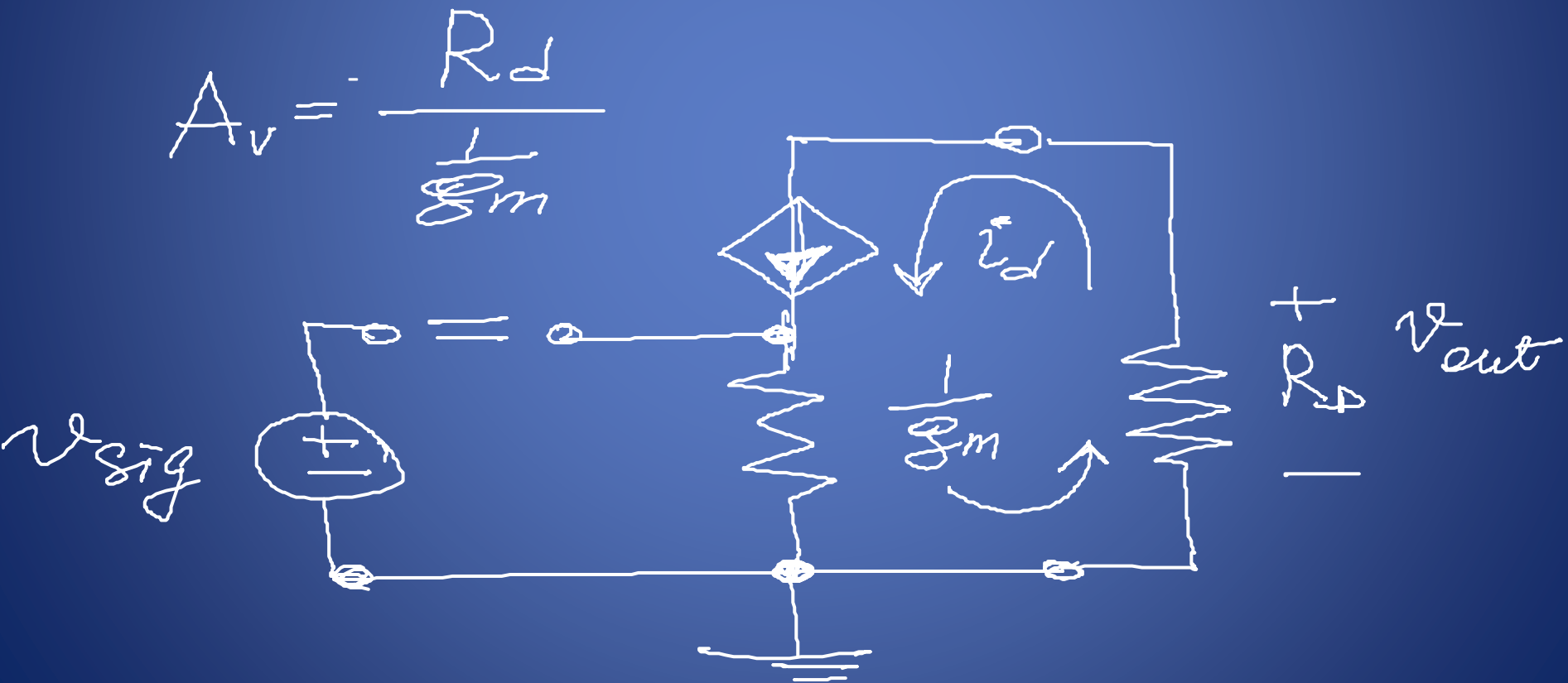Voltage gain is defined by RATIO of the EQUIVALENT
resistances in the DRAIN and SOURCE networks



BJT transconductance

$$g_m = \frac{\partial I_C}{\partial V_{BE}} = \frac{I_S}{V_T} \exp\left(\frac{V_{BE}}{V_T}\right) = \frac{I_C}{V_T}$$

$$g_m = \frac{I_C}{V_T}$$

$$g_m = \frac{180 \mu A}{26 mV} = 7 \frac{mA}{V}$$

At the same bias current
the BJT has much greater g_m
compared to the MOSFET

