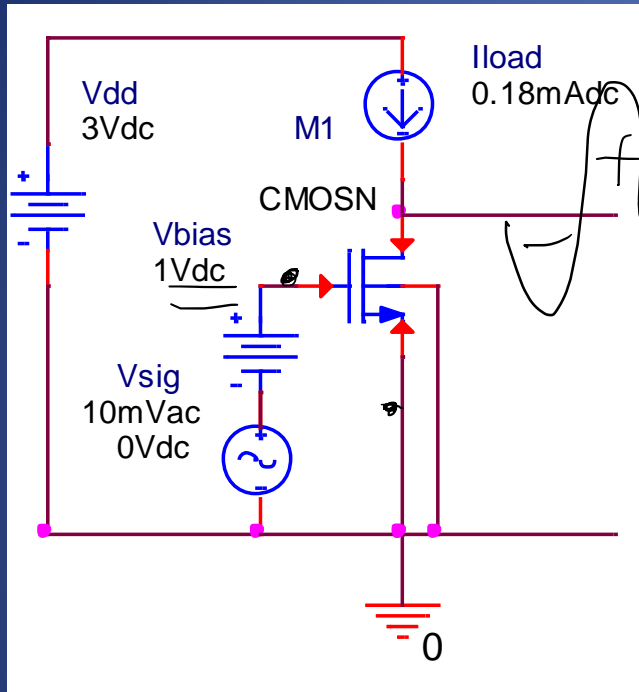


# Unit 8. Intrinsic gain

## Outline

1. MOSFET intrinsic gain
  - \* Design strategies for improving the voltage gain of a MOSFET stage
  - \* Strong inversion vs Weak inversion limits
2. BJT intrinsic gain

# Improving Intrinsic Gain $A_o = g_m r_o$



How to select the MOSFET parameters and the bias current to obtain a greater voltage gain?

Increasing product

$$g_m = \frac{2I_D}{V_{ov}} ; r_o = \frac{V_A}{I_D}$$

$$A_o = \frac{2I_D}{V_{ov}} \cdot \frac{V_A}{I_D} = \frac{2V_A}{V_{ov}} \cdot \frac{f_D}{f_{D0}}$$

\* Decreasing  $V_{ov}$ !  $\approx 130$

\* Increasing  $L$  for  $V_A \uparrow$

\* Increasing  $W$  for  $V_{ov} \downarrow$

\* Decreasing  $I_D$  for  $V_{ov} \downarrow$

$$A_o = \frac{2V_A' L}{V_{ov}}$$

# Improving voltage gain


$$A_o = 2 \frac{V_A' \cdot L}{V_{ov}}$$

(1)  $I_D = \text{const.}$ :  $A_o \propto \sqrt{W}$  ( $V_{ov} \propto \frac{1}{\sqrt{W}}$ )  
 $A_o \propto \sqrt{L}$  ( $V_A \propto L$ ,  $V_{ov} \propto \sqrt{L}$ )

(2)  $\left. \begin{array}{l} W = \text{const} \\ L = \text{const} \end{array} \right\} A_o \propto \frac{1}{\sqrt{I_D}}$  ( $V_{ov} \propto \sqrt{I_D}$ )


How small can  $V_{ov}$  be made?
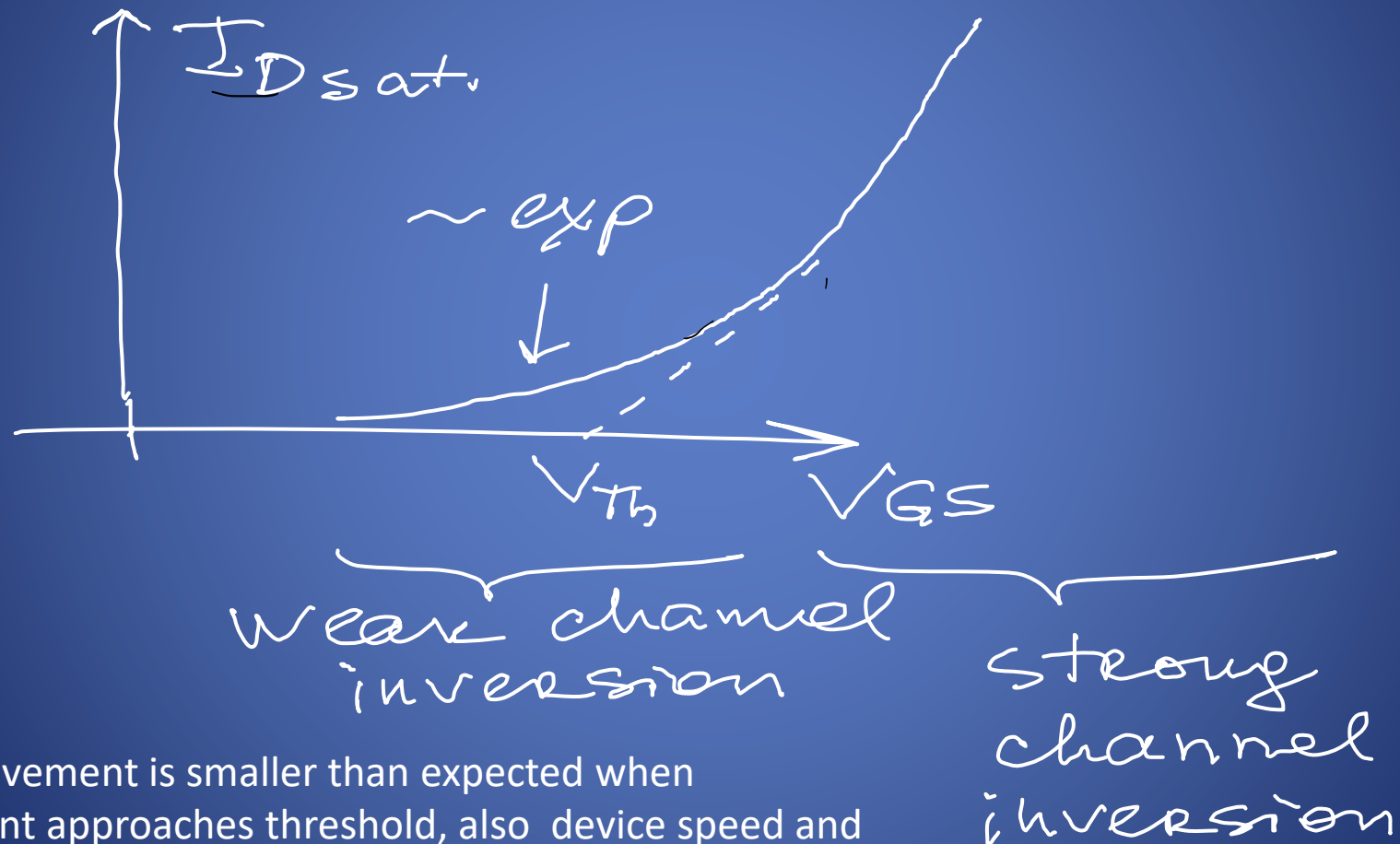
# MOSFET transfer characteristic near threshold



Improvement is smaller than expected when current approaches threshold, also device speed and range of  $V_{sig}$  decrease  $\Rightarrow$  typically  $V_{ov} = 0.1-0.3$  V

# Intrinsic gain versus bias current

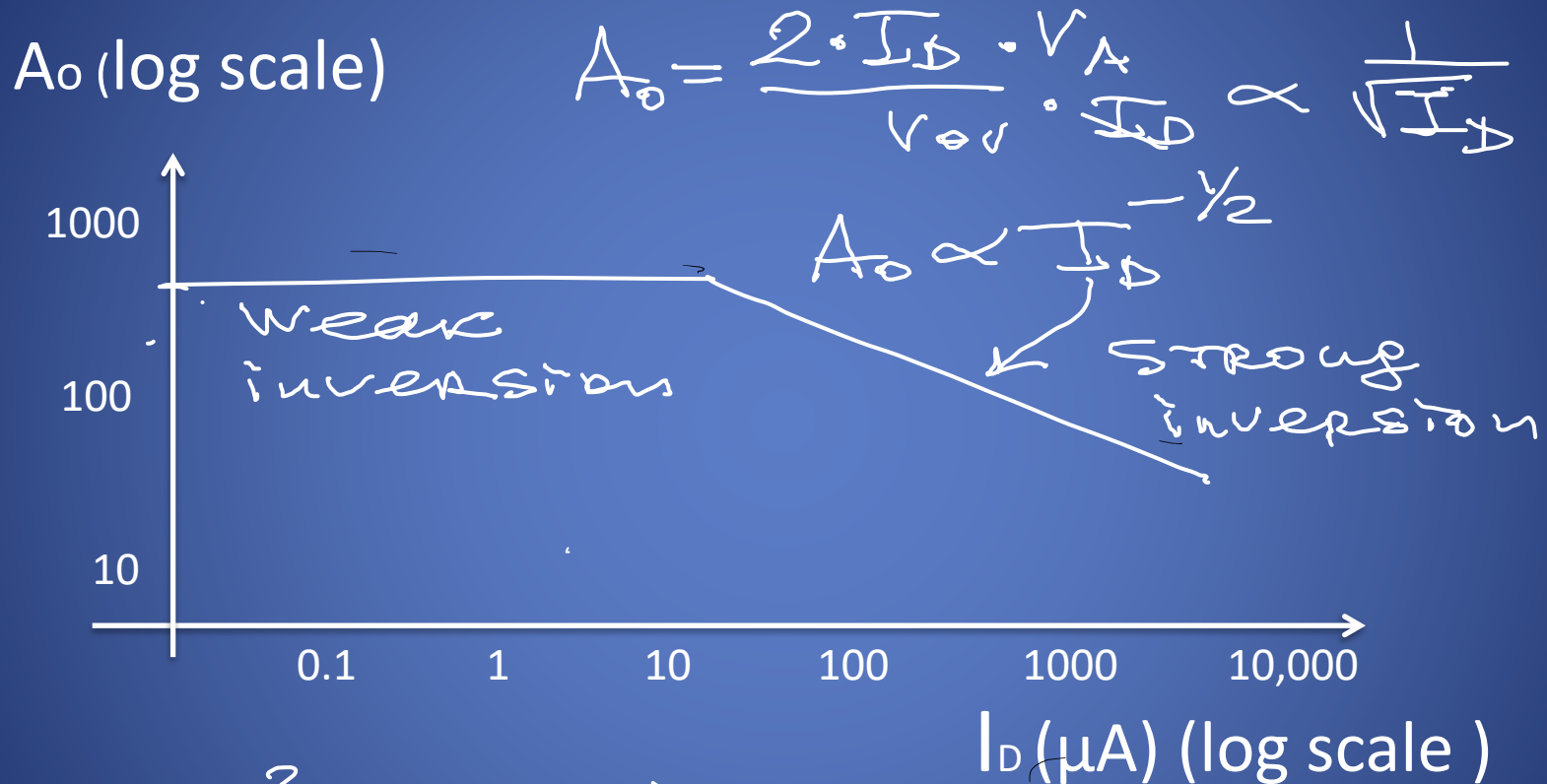

Selection of small current will degrade response time (frequency range)  
because a greater time will be needed to charge capacitances

# MOSFET intrinsic gain

$$1) \frac{W}{L} = 20; k_n' = 200 \frac{\mu A}{V^2}; V_{ov} = 0.1 V; V_A = 10 V$$

The intrinsic gain is expected to be a factor of 3 greater compared to the previous example with  $V_{ov} = 0.3 V$ , indeed

$$A_0 = \frac{V_A}{V_{ov}/2} = \frac{10}{0.05} = 200$$

$$2) \frac{W}{L} = 5, A_0 = \frac{10}{0.1} = 100$$

$$I_D \propto \frac{W}{L} V_{ov}^2 \rightarrow V_{ov} \uparrow \text{ by a factor of } 2 \\ V_{ov} = 0.2 V$$



# BJT intrinsic gain

$$A_0 = g_m r_o = \frac{\cancel{I_C}}{V_T} \cdot \frac{V_A}{\cancel{I_C}} = \frac{V_A}{V_T}$$

Intrinsic gain does not depend on current, however it is much more sensitive to temperature change compared to MOSFET

$$V_A = 35V \text{ (npn)}$$

$$A_0 = \frac{35}{26 \cdot 10^{-3}} = 1350!$$

$$V_T = \frac{k_B T}{e} = \frac{1.38 \cdot 10^{-23} \cdot 300}{1.6 \cdot 10^{-19}} = 0.026V$$

$$k_B = 1.38 \cdot 10^{-23} \text{ J/K (Boltzmann const)}$$

$$e = 1.6 \cdot 10^{-19} \text{ C (charge of electron)}$$