

## Unit 9

# n-MOSFET Common-Source amplifier with p-MOSFET current source load: selection of W and L

High voltage gain requires high load impedance

p-MOSFET to replace Load resistor

Rule of thumb selection of matched impedances of nMOS (pull down) and pMOS (pull up) networks:

$$r_{on} = r_{op} = r_o \Rightarrow R_{out} = r_o/2$$

Matched Early voltages of nMOS and PMOS devices

$$V_{an} = V_{ap}$$

$$L_p = 2 \times L_n$$



pMOSFET gate length doubled compared to that for nMOSFET

# A good current source has large $R_{out}$ , it can be obtained with large $V_{DD}$ and large $R$

Target: generation of 200  $\mu$ A DC  
(ideally independent from output voltage)

Possible solution: large  $V_{DD}$  (20V DC) in series  
with large  $R$  (100 k $\Omega$ )


*Current source*

  

n-MOSFET stage loaded with a large  $R = 100 \text{ k}\Omega$  would have large  
AC voltage gain:  $A_v = g_m R = 1.2 \text{ mA/V} \times 100 \text{ k}\Omega = 120$

# n-MOS stage loaded with p-MOS current source

$$|A_v| = g_m \cdot R_{out}$$

 

The voltage gain for AC signal is limited by the equivalent output resistance ( $R_{out}$ ) defined by connected in parallel  $r_{on}$  and  $r_{op}$ . Why in parallel?  $V_{DD}$  is a constant voltage source, in small signal equivalent circuit  $V_{DD}$  represents a short circuit. For AC signal DC source  $V_{DD}$  is equivalent to ground.

# Selection of gate length L for p-MOSFET

since  $R_{out} = r_{on} \parallel r_{op}$ , ideally, we would like to see  $r_{op} \gg r_{on}$ ,

The latter would require a pMOSFET with a long gate length  $L_p$  and a very wide pMOSFET  $W_p$ , respectively (for given overdrive voltage  $V_{ovp}$ )


One can select  $r_{on} = r_{op}$  for a reasonable width  $W_p$ .

Both nMOS and pMOS have the same DC current  $I_{Dn} = I_{Dp} = I_D$ , therefore

$$V_{A_n} = V_{A_p}$$


↓

$$L_p = 2 L_n$$

 

The gate length of p-MOS in the current source is selected to be  $\sim$ twice greater than  $L$  for the amplifying n-MOS transistor to compensate for relatively small Early voltage parameter of p-MOS  $V'_{Ap} = 10 \text{ V}/\mu m$  compared to that for n-MOS  $V'_{An} = 20 \text{ V}/\mu m$ .

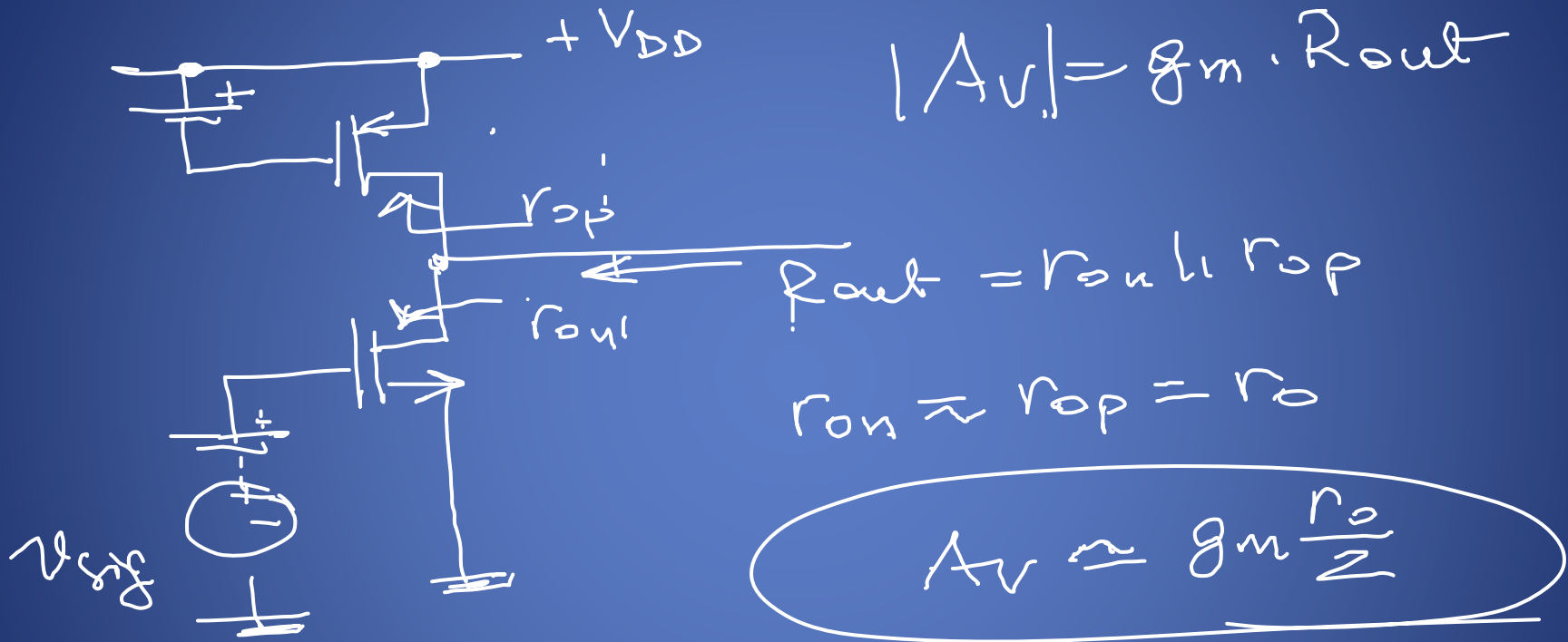Selection of  $r_{op} = r_{on}$  is a good compromise which combines a respectfully-high voltage gain of  $A_0/2$  with a not-too-wide p-MOSFET




In the case of  $r_{op} \ll r_{on}$ , the voltage gain would be limited by a small  $r_{op}$ , not good. Meeting condition  $r_{op} \gg r_{on}$  implies large  $L_p$  which leads to large  $W$  for the given drain current and overdrive voltage. This would be a too expensive solution due to large p-MOSFET size. Selection of the design parameters for matching output resistances ( $r_{op} = r_{on}$ ) is a reasonable compromise which achieves both moderate voltage gain (only twice smaller than  $A_0$ ) and moderate  $W$  of the p-MOSFET load. 5


 
# p-MOSFET current source as n-MOSFET load in the voltage gain stage

The LOAD LINE represents an output characteristic of p-MOSFET with high load resistance for AC signal




Operating point or quiescent (Q)-point):  
 $V_D^* = 1.5V$ ,  $I_D^* = 200 \mu A$

The maximum output voltage (peak)  $V_{out \text{ max}}$  is smaller than  $V_{DD}$  by the p-MOSFET overdrive voltage  $V_{ovp}$   
 $V_{out \text{ max}} = V_{DD} - V_{ovp} = 3 - 0.3 = 2.7 \text{ V}$

The voltage scale reflects  $V_D$  measured with respect to ground  
 $V_D$  increases to the right from 0 to  $V_{DD} = +3V$  DC.
 
# DC Operating point and selection of the pMOSFET bias ( $V_{gs}$ and $V_{ov}$ , respectively)



The stage operating point ( $V_D^*$ ,  $I_D^*$ ) is defined by intersection of the output characteristics of n-MOS and p-MOS devices. The optimal position of the operating point is  $V_D^* = V_{DD}/2$  for the maximum amplitude of undistorted output voltage.

With small slopes of the output characteristics, the operating point is very sensitive to selection of MOSFET design parameters:  $V_{ovn}$ ,  $V_{ovp}$ , as well as  $W$  and  $L$ .

# Selection of the aspect ratio for p-MOS

by default  $I_{Dn} = I_{Dp}$

Requesting symmetrical clipping of the output voltage implies  $V_{ovn} = V_{ovp}$

It would lead to a very wide p-MOSFET

$$W_p = (k'_n/k'_p) * (V'_{An}/V'_{Ap}) * W_n = 6 W_n$$

$$\frac{k'_n}{k'_p} = 3$$

$$\frac{V'_{An}}{V'_{Ap}} = 2$$

A wide p-MOSFET current source would take too much area,  
and would create a large capacitive load for n-MOSFET stage

For given DC current,  $W$  changes as a square of  $V_{ov}$ .  $V_{ovp}$  can be moderately increased (x1.4 times) for significant (x2 times) decrease of  $W_p$ .

The width of p-MOSFET would be reasonably wider than that of n-MOSFET:  $W_p = 3 W_n$  realized with matched output resistances of n-MOS and p-MOS transistors ( $L_p = 2 * L_n$ )



# Summary of (most important) expressions

Selection of overdrive voltage and DC bias voltage:

$$V_{ov} = V_{GS} - V_t \rightarrow V_{GS}$$

Transconductance and selection of DC bias current:

$$g_m = 2I_D/V_{ov} \rightarrow I_D$$

Output resistance and gate length:

$$r_o = V_A/I_D = (V'_A * L)/I_D \rightarrow L$$

Aspect ratio and MOSFET width:

$$(W/L) = (2I_D)/(k' * V_{ov}^2) \rightarrow W$$

High output resistance  $r_o$  can be realized with a long gate length  $L$

The long gate length  $L$  implies a large mosfet width  $W$

$K'_p < k'_n \rightarrow$  for moderate width of p-MOSFET (and other reasons TBD) one selects  $V_{ovp} > V_{ovn}$

# Summary of (most important) process and design parameters

## Process parameters

### 1. Threshold voltages

$$V_{tn} = 0.7 \text{ V}, V_{tp} = -0.8 \text{ V}$$

### 2. Process transconductance parameters

$$k_n' = 200 \text{ } \mu\text{A/V}^2, k_p' = 70 \text{ } \mu\text{A/V}^2$$

### 3. Early voltage parameters

$$V_{An}' = 20 \text{ V/}\mu\text{m}, V_{Ap}' = 10 \text{ V/}\mu\text{m}$$

## Design parameters

$$V_{ovn} = 0.2 \text{ V}, |V_{ovp}| = 0.3 \text{ V}$$

DC bias current:  $I_D$

Gate lengths:  $L_n, L_p$

Gate widths:  $W_n, W_p$