

## EEO 311

### Quiz 6

Pete Mills

March 31, 2024

- 1 What would be the DC gain of the 2-stage circuit in dB units?

Find total gain  $AV_{total}$

$$AV_{total} = AV_1 \cdot AV_2$$

$$AV_{total} = 10 \cdot 10 = 100$$

$$AV_{total} = 20 \log(100) = 40 \text{ dB}$$

- 2 A sinusoidal voltage with the amplitude of 1 mV and a 100 MHz frequency was applied to the input of the 1st stage of the circuit. What would be the amplitude of the output voltage of the 2-stage circuit?

Find  $V_{out}$

$$V_{out} = V_{in} \cdot \left(\frac{1}{\sqrt{2}} \cdot AV_1\right) \cdot \left(\frac{1}{\sqrt{2}} \cdot AV_2\right)$$

$$V_{out} = 1 \text{ mV} \cdot \left(\frac{1}{2} \cdot 100\right) = 50 \text{ mV}$$

- 3 What would be the cut-off frequency of the 2-stage circuit in MHz at the -3 dB level?

$$f_{c,2\text{-stage}} = \frac{1}{\sqrt{2}} \times f = 0.707 \times 100 \text{ MHz} = 70.7 \text{ MHz}$$

- 4 What would be the phase angle of the transfer function of the 2-stage circuit at the cut-off frequency?

Phase shifts are summed in series-connected LPF's. Each Stage is introducing  $-45^\circ$ , therefore a total phase shift of  $-90^\circ$  is seen at the output.