

## EEO 352 Fall 2023 - Assignment 4 – Digital Gates

Please document each step with snapshots of the built circuit, plots, pictures and your observations. Please include this page.

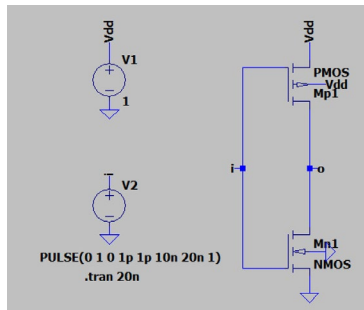


Fig.1a

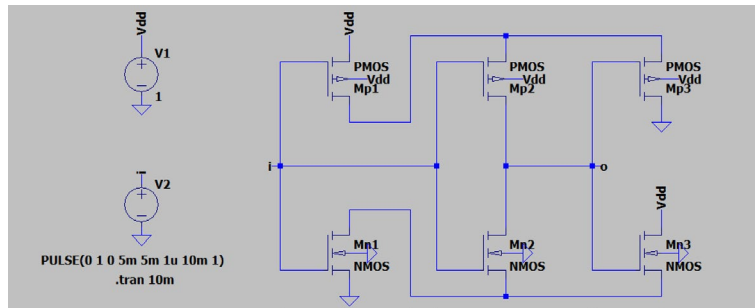


Fig.1b

### 1) Design and simulate as follows (50pts):

- CMOS inverter, as shown in Fig.1a using the nmos4 and pmos4 ideal parts:
  - using a pulse waveform simulate and plot the input and output
  - using a 100Hz triangular waveform plot the input and output and extrapolate and report the threshold voltages at 50% of the output swing
  - replace the ideal MOSFETs (right-click on the parts) with the Si7540DP-P/N, increase the voltages to 5V, plot the input and output, extrapolate the delays (1ns input edges) and extrapolate the thresholds (10Hz triangular waveform)
- CMOS Schmitt trigger, as shown in Fig.1b using the nmos4 and pmos4 ideal parts:
  - using a pulse waveform simulate and plot the input and output
  - using a 100Hz triangular waveform plot the input and output and extrapolate and report the threshold voltages at 50% of the output swing
- NAND and NOR gates using the nmos4 and pmos4 ideal parts:
  - simulate and plot (use three plot panes) the inputs and output
- XOR gate using four ideal NAND parts (inverted output of the AND part) in the Digital library:
  - simulate and plot (use three plot panes) the inputs and output
- XOR gate using four ideal NOR parts (inverted output of the OR part) and one inverter:
  - simulate and plot (use three plot panes) the inputs and output

Note1: when using the Si7540DP please replace the nmos4 and pmos4 with nmos and pmos first; note that the bulk gets internally connected with the source.

Note2: the ideal parts in the Digital library nominally operate between 0V and 1V, the Si7510DP operate between 0V and 5V

### 2) Using the CD4007 CMOS array, build and measure (115 pts):

- The circuit at (1a), measuring the delays and the threshold voltages and plotting the corresponding inputs and outputs
- The circuit at (1b), measuring the delays and the threshold voltages and plotting the corresponding inputs and outputs
- The two circuits at (1c), using one 1kHz 5V square wave and one 500Hz square wave, plotting the 500Hz input and the output

Note1: CD4007 requires supply and signal voltages as per datasheet, 5V recommended.

### 3) Using the 74LS00 NAND array, build and measure (35 pts):

- The circuit at (1d), using one 2kHz 5V square wave and one 1kHz square wave, plotting the input and the output