

EEO352 Lab 8
Bipolar Junction Transistors (BJTs)

Pete Mills

November 27, 2023

Copy of Original Assignment

EEO 352 Fall 2023 - Assignment 8 – Bipolar Junction Transistors (BJTs)

Please document each step with snapshots of the built circuit, plots, pictures and your observations.
Please include this page.

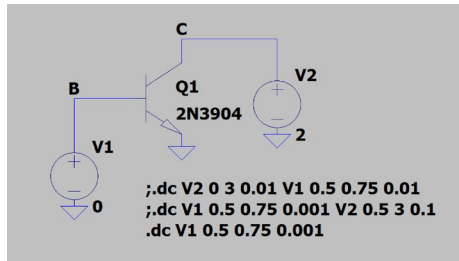


Fig.1

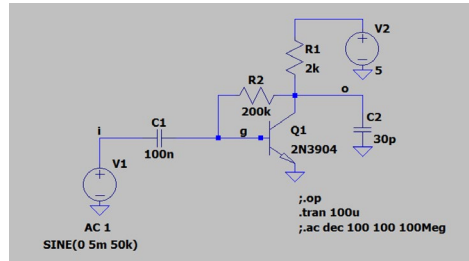


Fig.2

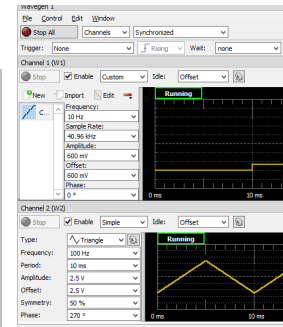


Fig.3

- 1) Using the npn BJT 2N3904 (pick from npn) as in Fig1 simulate and plot the following **(25pts)**:
 - a) Collector current I_c vs V_{ce} (range 0V to 3V) with parametric V_{be} (0.5V to 0.75V, 10mV steps)
 - b) Collector current I_c vs V_{be} (range 0.5V to 0.75V) with parametric V_{ce} (0.5V to 3V in 100mV steps)
 - c) Collector current I_c vs V_{be} (range 0.5V to 0.75V) at $V_{ce}=2V$, and extrapolate the V_{be} at $I_c=1mA$
 - d) Derivative ($d(I_c)/d(V_{be})$) of the collector current I_c vs V_{be} (range 0.5V to 0.75V) at $V_{ce}=2V$, and extrapolate the transconductance at $I_c=1mA$
 - e) Current gain I_c/I_b vs V_{be} (range 0.5V to 0.75V) at $V_{ce}=2V$, and extrapolate the gain at $I_c=1mA$
- 2) Using the npn BJT 2N3904, one $2k\Omega$ resistor at the collector, and one $200k\Omega$ to bias the base, build the amplifier in Fig.2 and simulate and plot the following **(25pts)**:
 - a) Response to 50kHz 5mV sinusoidal signal (plot in separate panes) and extrapolate the gain
 - b) Frequency response, extrapolating the gain and -3dB bandwidth without and with a 30pF load
- 3) Using the npn BJT 2N3904, one 100Ω resistor at the collector and one $10k\Omega$ resistor at the base (between the base and the applied voltage), build and plot **(75pts)**:
 - a) Collector current I_c vs V_{ce} (range 0V to 3V) with parametric V_{be} (see example in Fig.3)
 - b) Collector current I_c vs V_{be} (range 0.5 to 0.75V) for $V_{ce}>2V$, and extract the V_{be} and the g_m at $I_c=1mA$
 - c) Gain I_c/I_b vs Collector current I_c (setting as in (b)) and extract the gain at $I_c=1mA$

Hint1: for (b) use W1 Triangle Amp=0.3V, Off=0.9V at the $10k\Omega$

Hint2: for (c) use connect C2 across the $10k\Omega$ and add Math I_c/I_b
- 4) Build and measure the amplifier in Fig.2 and plot the following **(75pts)**:
 - a) Response to 50kHz 5mV sinusoidal signal and extract the gain
 - b) Frequency response, extracting the gain and the -3dB bandwidth

Hint1: for (b) use the minimum signal amplitude

Summary

In this lab we ...

1 Simulate and Measure Circuit 1

a)

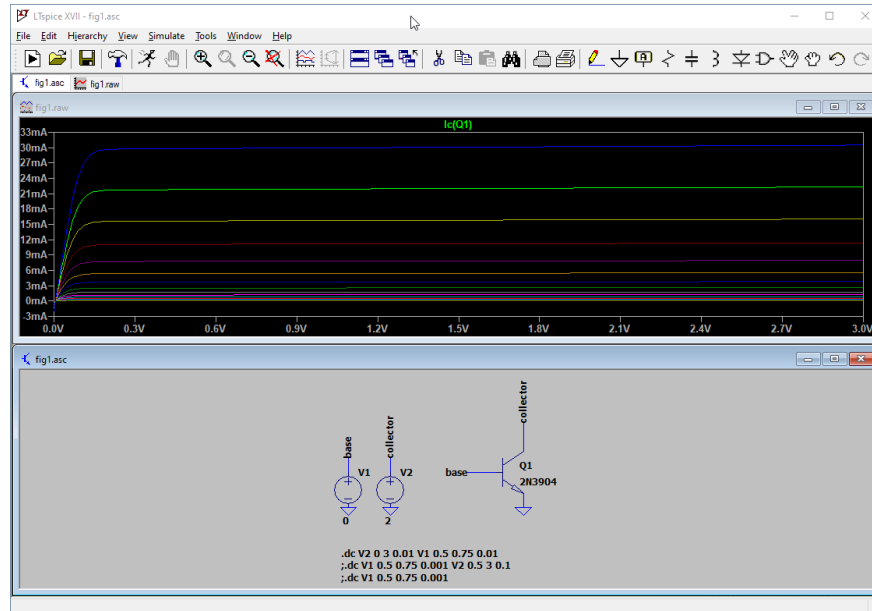


Figure 1: Collector current I_c vs V_{ce} (range 0V to 3V) with parametric V_{be} (0.5V to 0.75V, 10mV steps)

b)

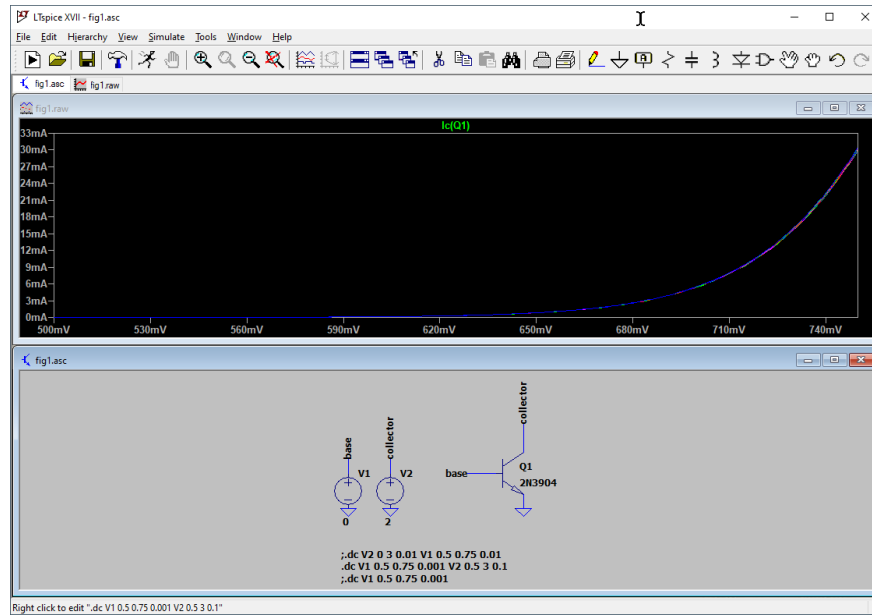


Figure 2: Collector current I_c vs V_{be} (range 0.5V to 0.75V) with parametric V_{ce} (0.5V to 3V in 100mV steps)

c)

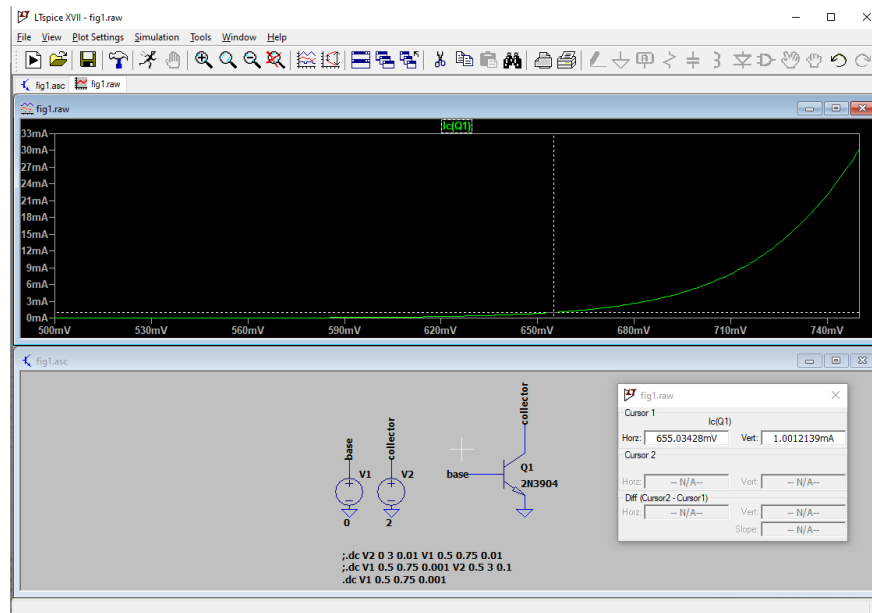


Figure 3: Collector current I_c vs V_{be} (range 0.5V to 0.75V) at $V_{ce}=2V$, and extrapolate the V_{be} at $I_c=1mA$

V_{be} is $\approx 655 \text{ mV}$ @ $I_c = 1 \text{ mA}$

d)

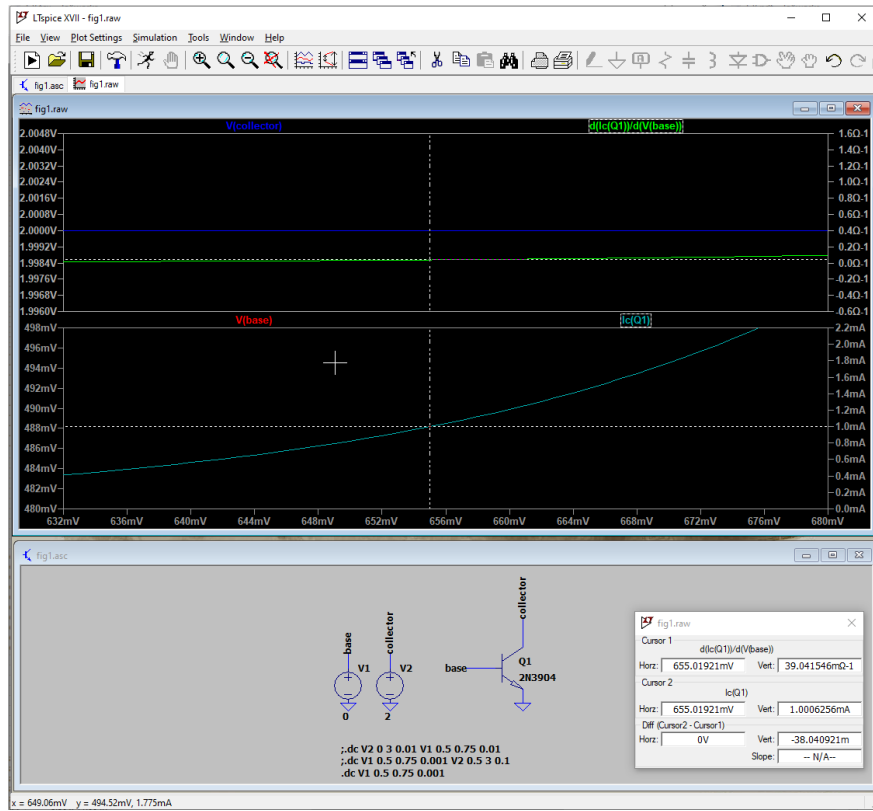


Figure 4: Derivative ($d(\cdot)$) of the collector current I_c vs V_{be} (range 0.5V to 0.75V) at $V_{ce}=2V$, and extrapolate the transconductance at $I_c=1mA$

The transconductance g_m is found to be $39.042 \text{ m}\Omega @ I_c = 1 \text{ mA}$

e)

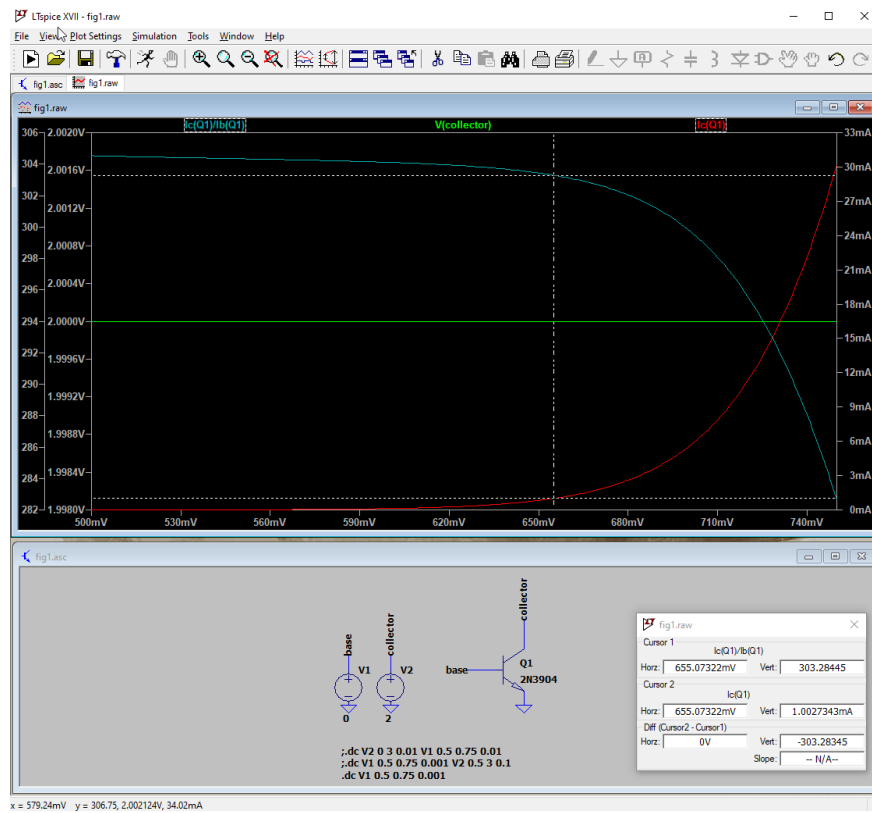


Figure 5: Current gain I_c/I_b vs V_{be} (range 0.5V to 0.75V) at $V_{ce}=2\text{V}$, and extrapolate the gain at $I_c=1\text{mA}$

The gain is ≈ 303.3

2 Simulate and Measure Circuit 2

a)

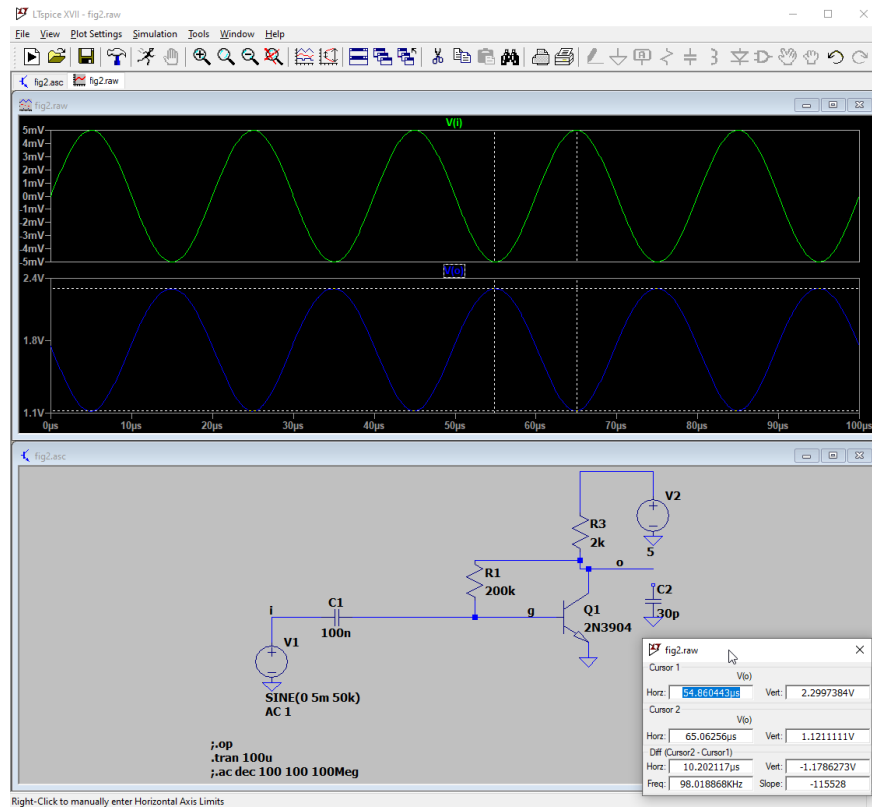


Figure 6: Response to 50kHz 5mV sinusoidal signal (plot in separate panes) and extrapolate the gain

The input amplitude is 5 mV pp and output amplitude is 1.179 V pp, centered about 1.77 V, therefore the gain is ≈ 236 .

b)

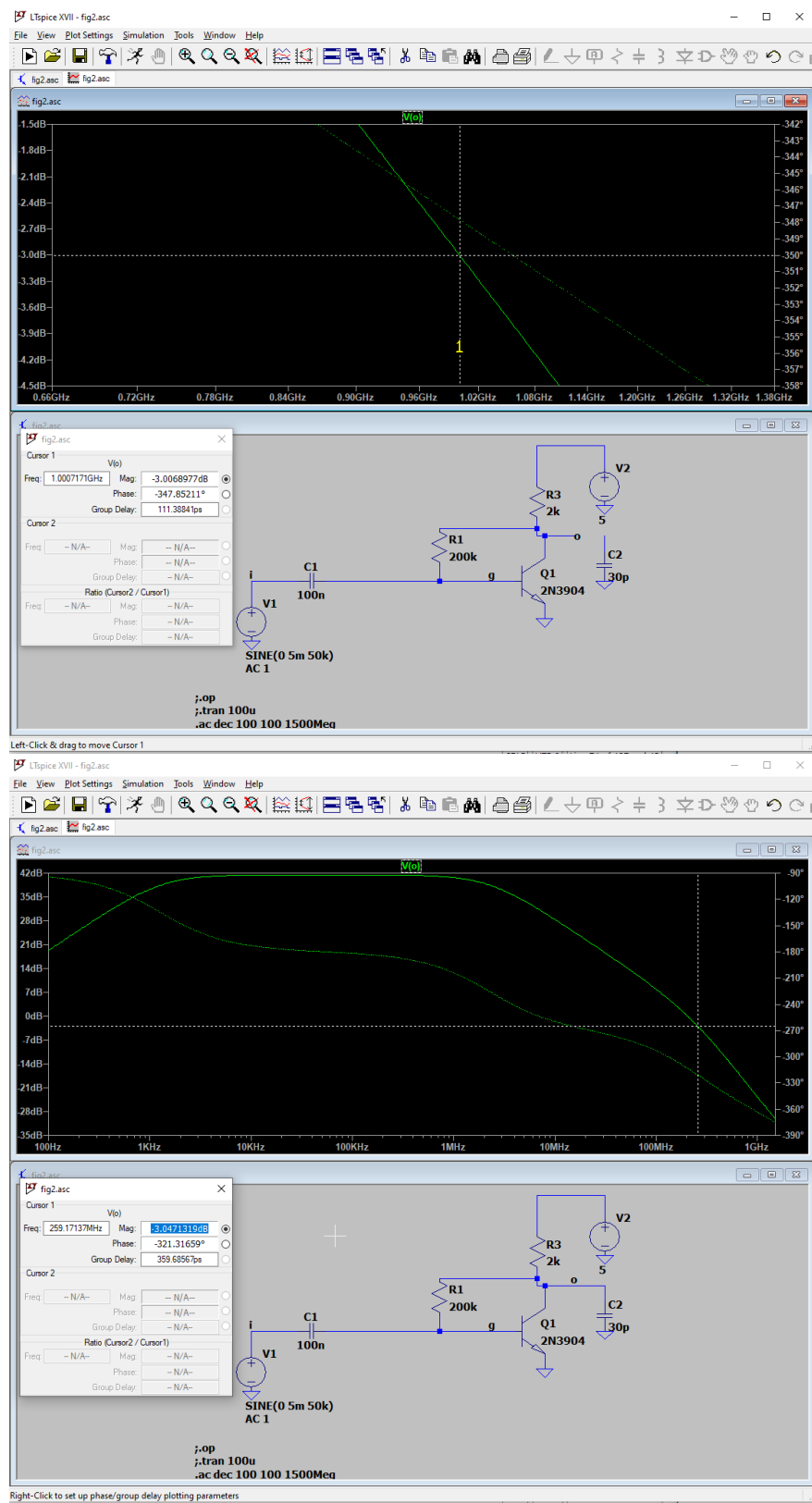


Figure 7: Frequency response, extrapolating the gain and -3dB bandwidth without and with a 30pF load

Without the 30 pF output capacitance, the -3 dB point is found at 1.0 GHz
With the 30 pF output capacitance, the -3 dB point is found at 259.2 MHz

3 Build and Measure Circuit 1

a)

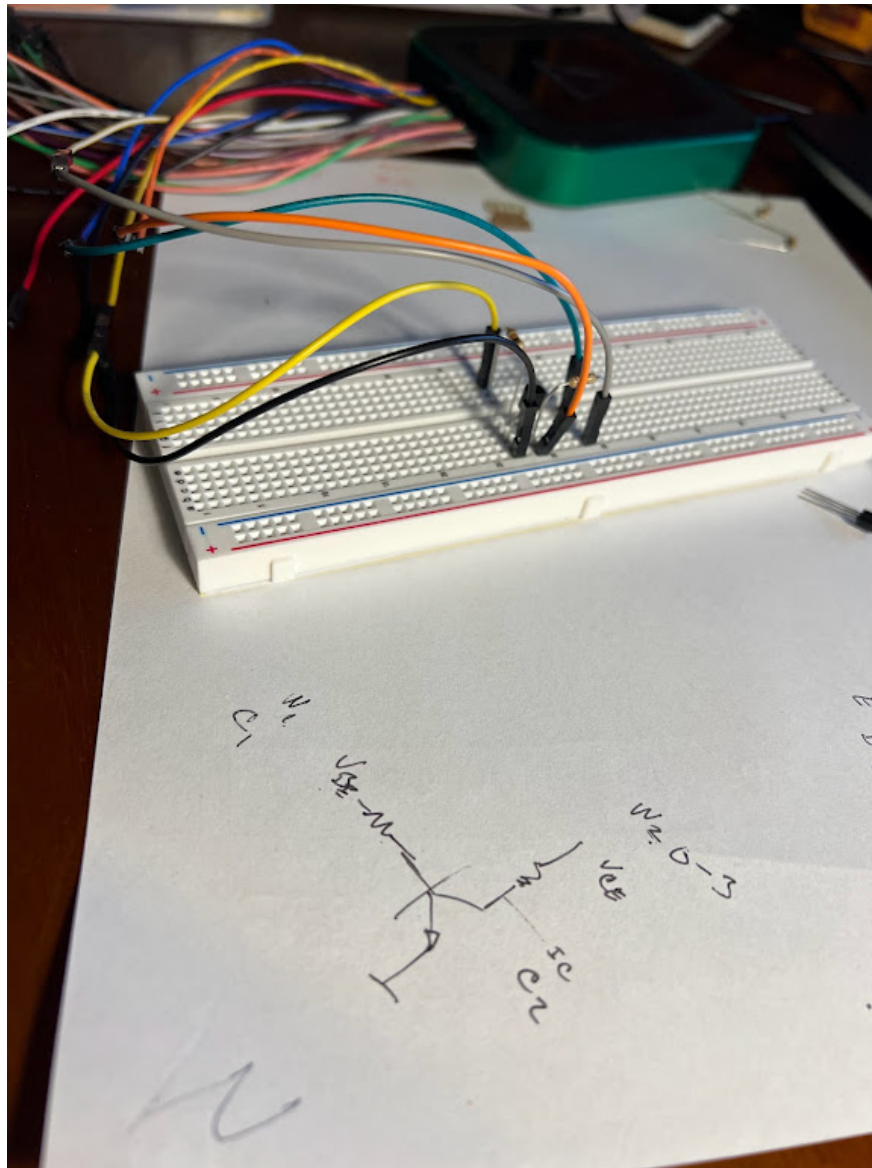


Figure 8: Test Setup

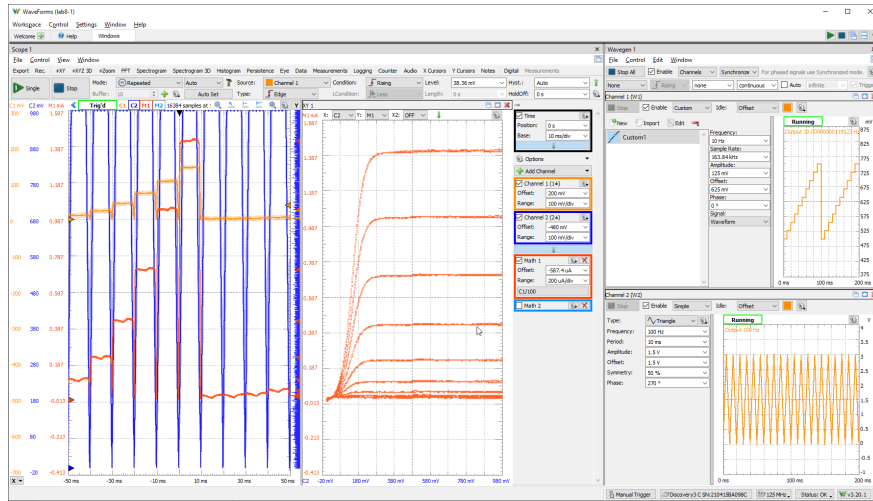


Figure 9: Collector current I_c vs V_{ce} (range 0V to 3V) with parametric V_{be} (see example in Fig.3)

b)

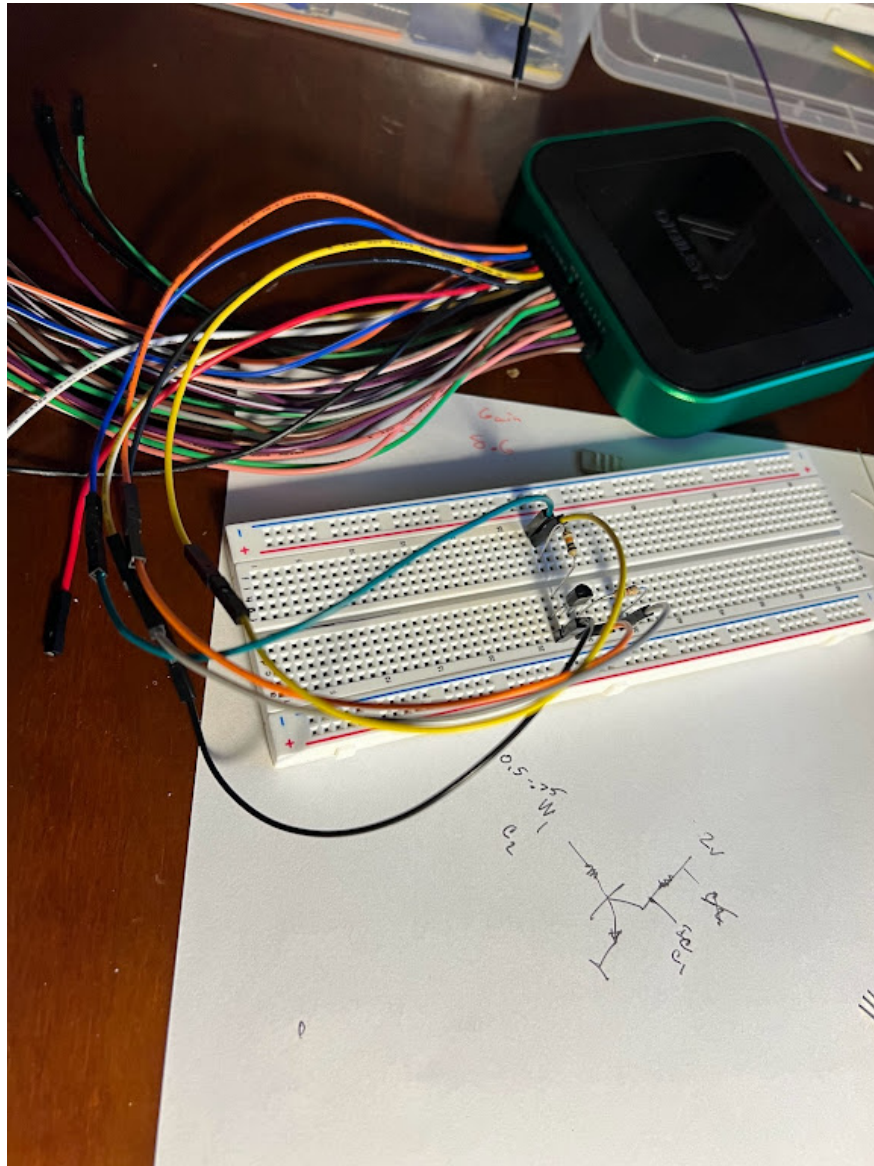


Figure 10: Test Setup

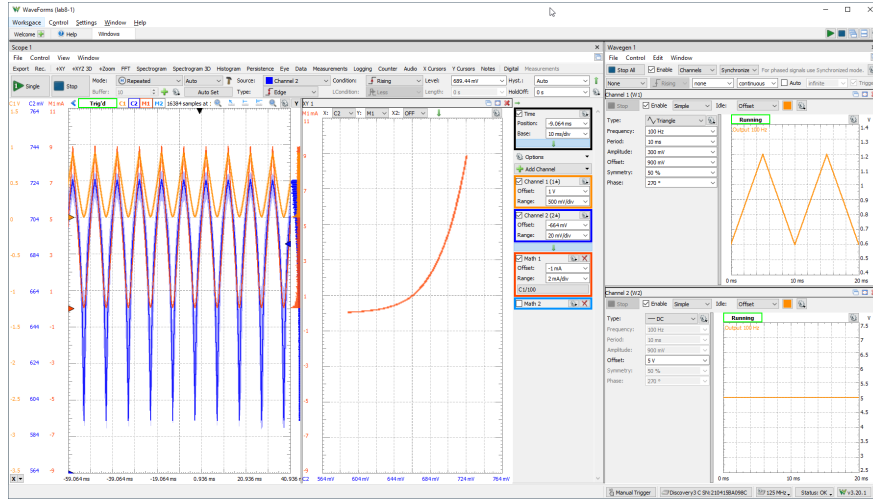


Figure 11: Collector current I_c vs V_{be} (range 0.5 to 0.75V) for $V_{ce}=2V$, and extract the V_{be} and the g_m at $I_c=1mA$

V_{be} is $\approx 664mV$ @ $I_c = 1mA$

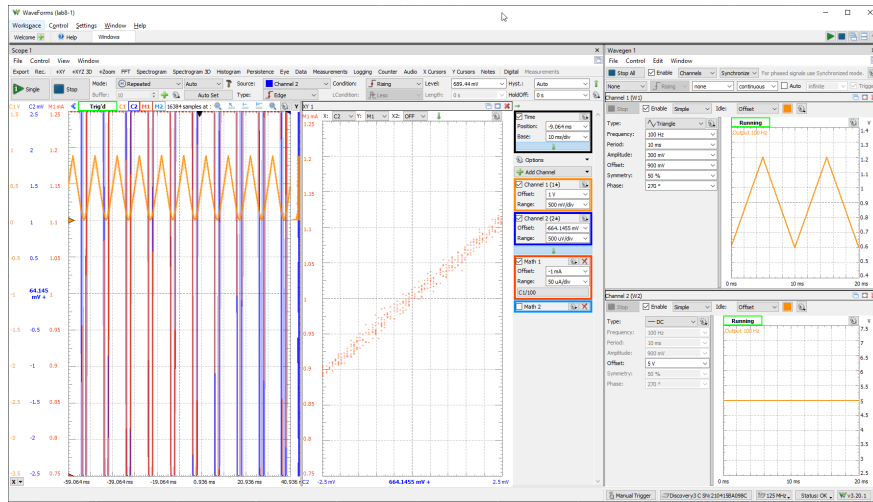


Figure 12: Zooming in to calculate $g_m = \Delta V / \Delta I$

At $I_c = 1mA$, $g_m \approx 25m\Omega$

c)

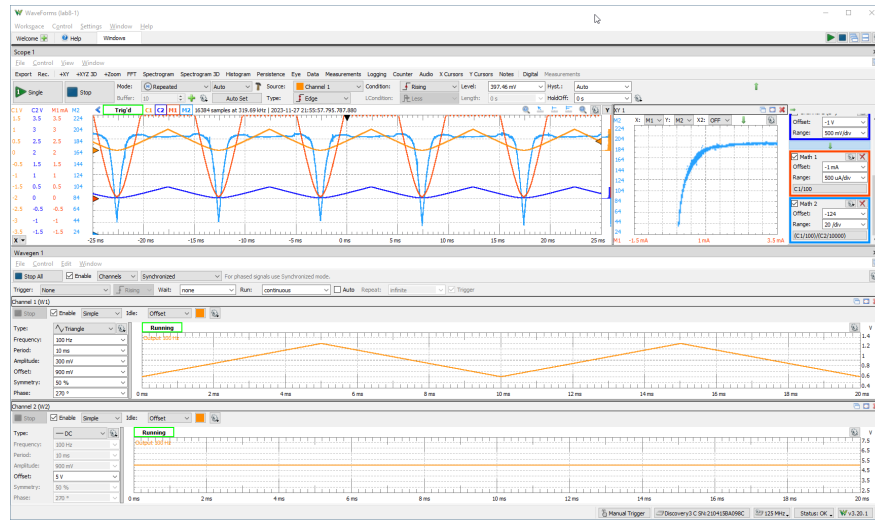


Figure 13: Gain I_c/I_b vs Collector current I_c (setting as in (b)) and extract the gain at $I_c=1\text{mA}$

The gain is found to be ≈ 180

4 Build and Measure Circuit 2

a)

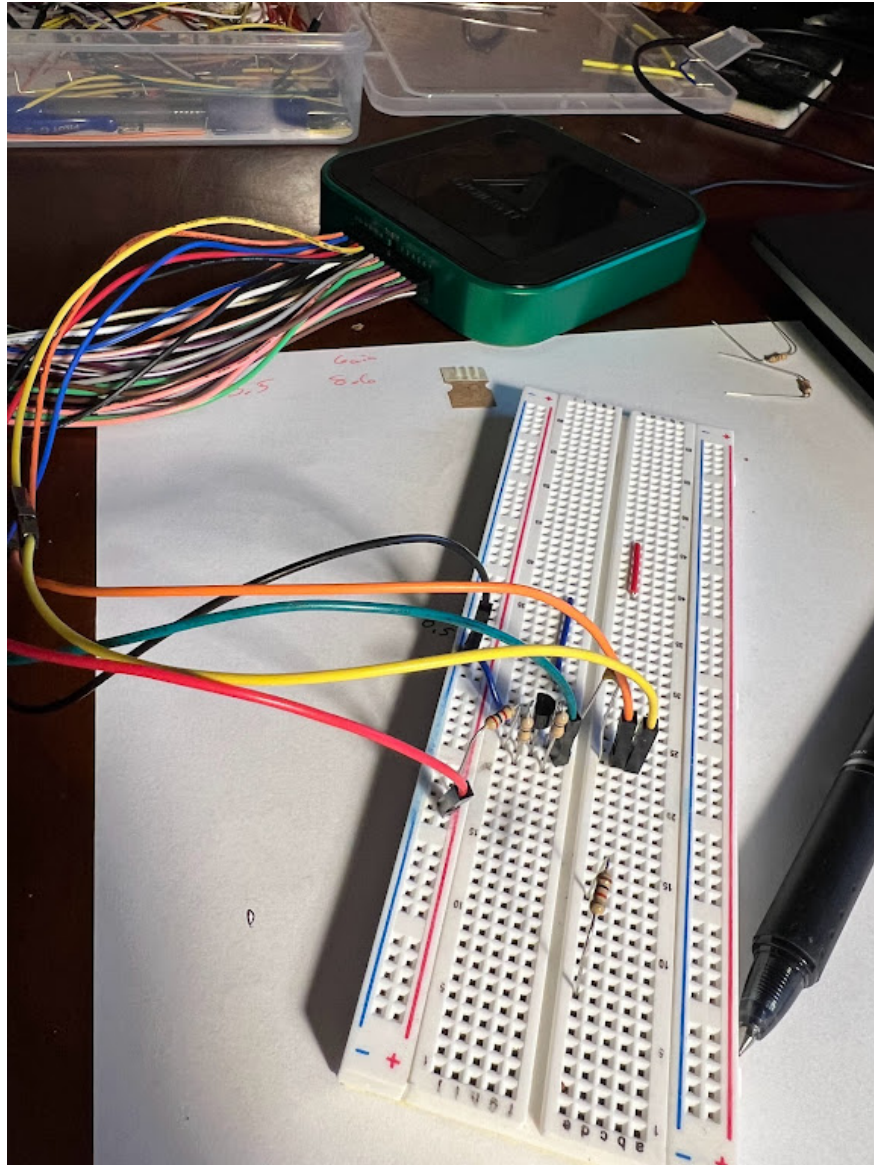


Figure 14: Test Setup

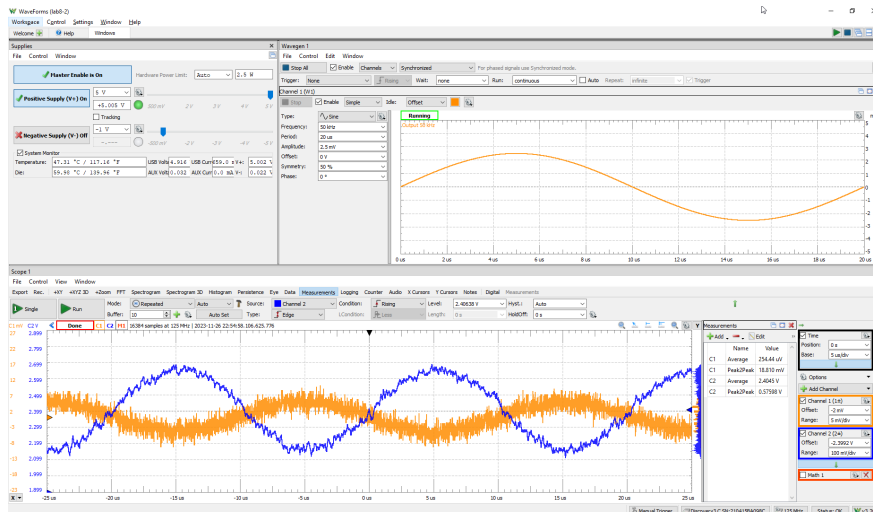


Figure 15: Response to 50kHz 5mV sinusoidal signal and extract the gain

The input amplitude is 5 mV pp and output amplitude is 0.57 V pp, centered about 2.4 V, therefore the gain is 114.

b)

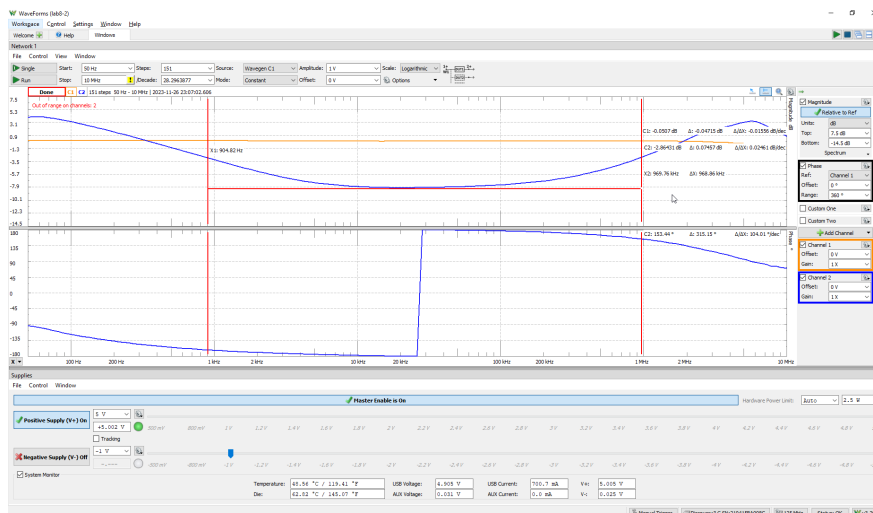


Figure 16: Frequency response, extracting the gain and the -3dB bandwidth

Using the Digilent Waveforms Network Analyzer it appears there is a -3dB point at about 900 Hz and another at at about 900 kHz. At the time of writing, I am not sure what this means, but will continue to research to understand.