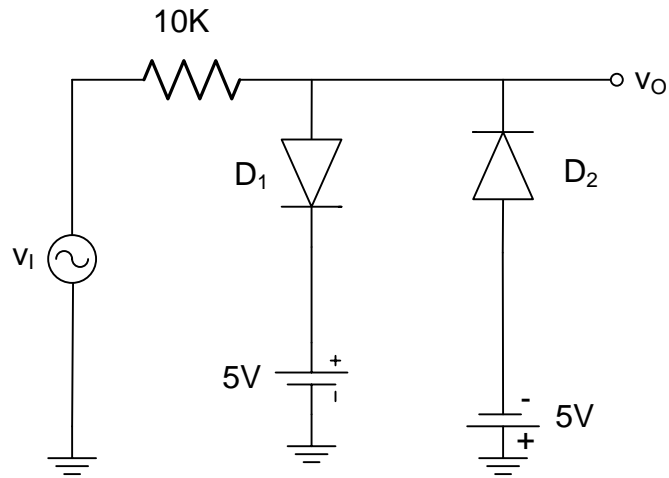


Problem 1


Consider the following circuit. Assume $V_\gamma = 0.7\text{V}$, $R_F = 0$, $v_I = 10\sin(2\pi 100t)\text{ V}$.



Plot the transfer function v_O versus v_I (v_I in the range from -10V to 10V).

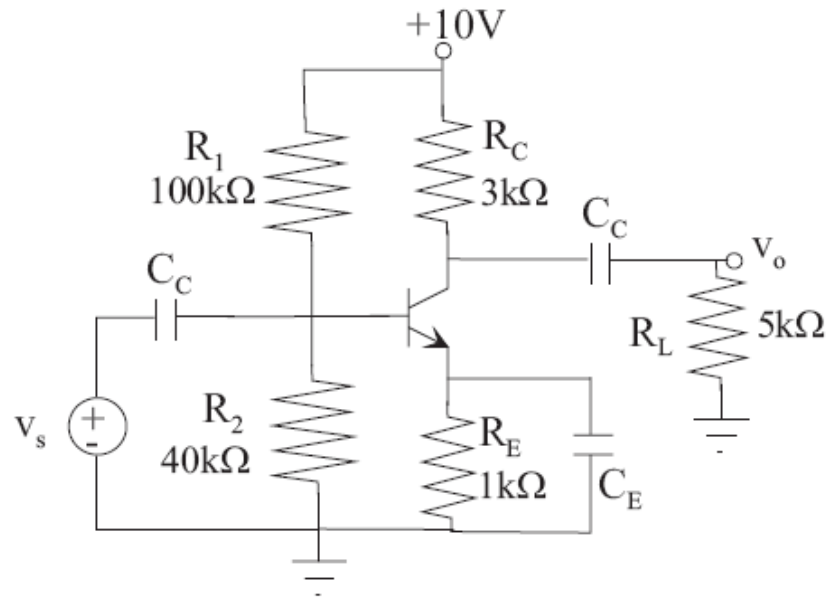Problem 2

In the following circuit, the transistor has $\beta = 120$ and $V_{BE(\text{on})} = 0.7\text{V}$.




- (5 points)** Determine the Q-point (I_C , V_{CE})
- (5 points)** Draw the dc and ac load lines.
- (5 points)** Draw the small-signal equivalent circuit.
- (5 points)** Determine the maximum symmetrical output voltage swing.
- (5 points)** Determine the input voltage v_s corresponding to the maximum swing in v_o .

Problem 3


Consider the following circuit. Assume $V_{TP} = -2V$, $K_p = 5mA/V^2$, $\lambda = 0.01 V^{-1}$, $R_G = 200k\Omega$, $R_L = 20k\Omega$, $I_Q = 0.5mA$

- (10 points) Determine I_D , V_{GS} , V_{DS} .
- (10 points) Draw the small-signal equivalent circuit and determine the output resistance R_o
- (5 points) Determine the voltage gain

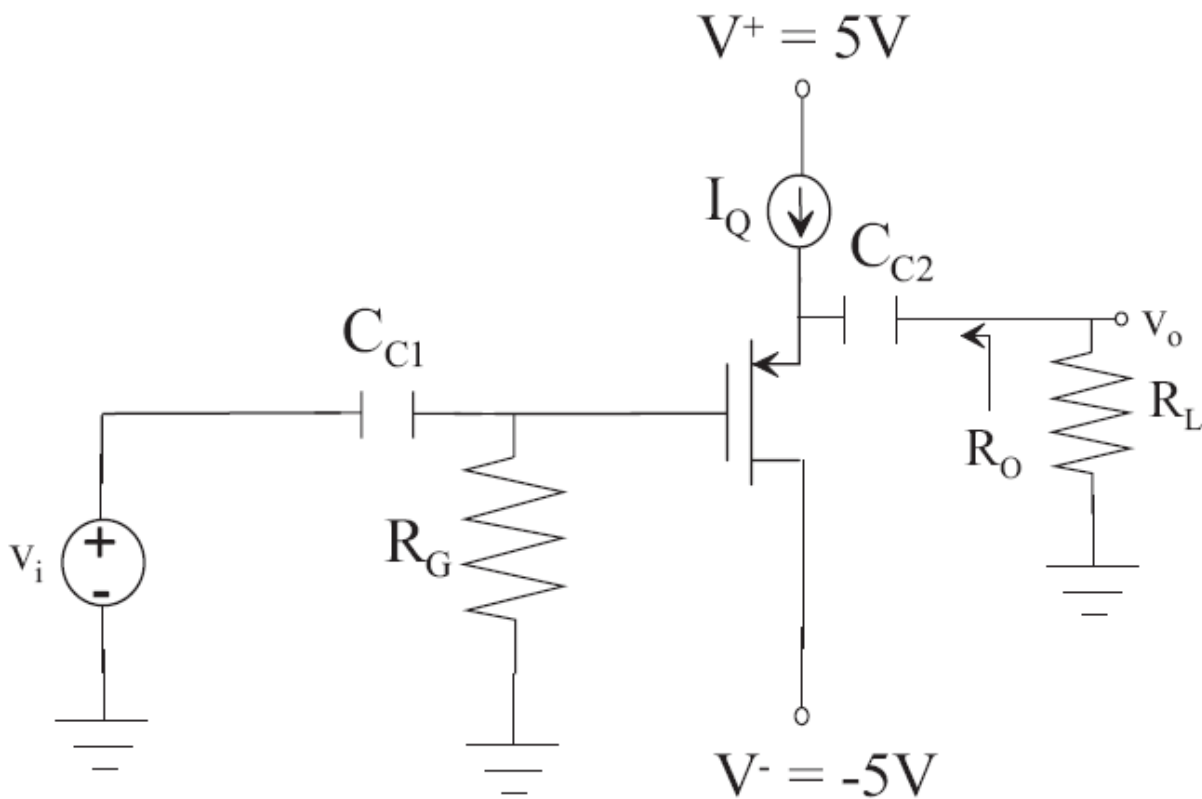

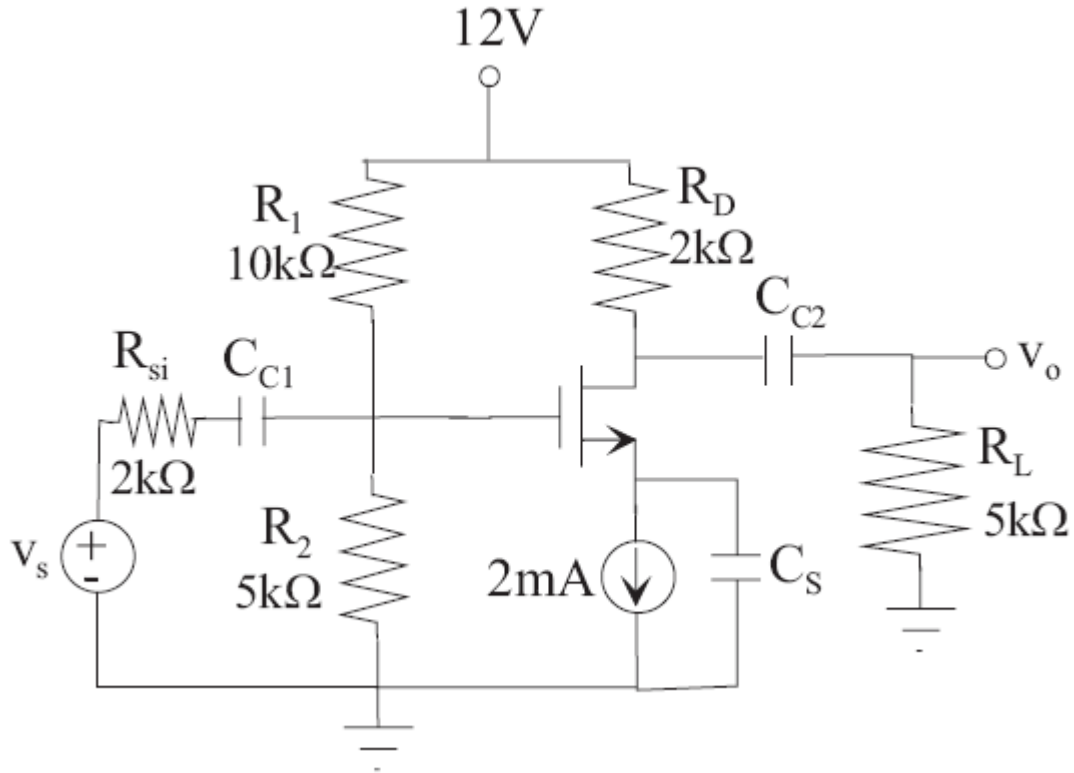Problem 4

In the following circuit, the transistor parameters are $V_{TN} = 2\text{V}$, $K_n = 2 \text{ mA/V}^2$, $\lambda = 0.01 \text{ V}^{-1}$



- (5 points) Determine I_D , V_{DS} , and V_{GS}
- (10 points) Draw the small signal equivalent circuit
- (10 points) Determine the voltage gain