

EEO 352 Lab 2

Pete Mills

TABLE I
SCORING TABLE

Item	Credit	Score
Low-pass or High-pass Filter		
Circuit Diagram with Values of Components	1	
Measured and Calculated Frequency Plot; -3dB Point	3	
Transient, Time Response	1	
Diodes		
I-V Plot	2	
Curve Fitting; IS, η	3	
Total	10	

Abstract—Abstract text here.