

# Unit 10

## Analysis and design Common-Source amplifiers with simple current source loads

Analysis of CS gain stages:  
Estimate  $R_{out}$ ,  $A_v$ , range of  $V_{out}$   
for given circuit parameters

1. n-MOSFET CS gain stage  
Impact of p-MOSFET current source  
gate length on voltage gain

2. p-MOSFET CS gain stage

Design of CS gain stages:  
Estimate circuit parameters ( $I_d$ ,  $W$ ,  
 $L$ ,  $V_{gs}$  for both MOSFETs) for  
specified  $R_{out}$ ,  $A_v$ ,  $V_{out}$  range

# Summary of (most important) process and design parameters

## Process parameters

### 1. Threshold voltages

$$V_{tn} = 0.7 \text{ V}, V_{tp} = -0.8 \text{ V}$$

### 2. Process transconductance parameters

$$k_n' = 200 \text{ } \mu\text{A/V}^2, k_p' = 70 \text{ } \mu\text{A/V}^2$$

### 3. Early voltage parameters

$$V_{An}' = 20 \text{ V/}\mu\text{m}, V_{Ap}' = 10 \text{ V/}\mu\text{m}$$

## Design parameters

$$V_{GS\_nmos}, V_{GS\_pmos}$$


DC bias current:  $I_D$

Gate lengths:  $L_n, L_p$

Gate widths:  $W_n, W_p$

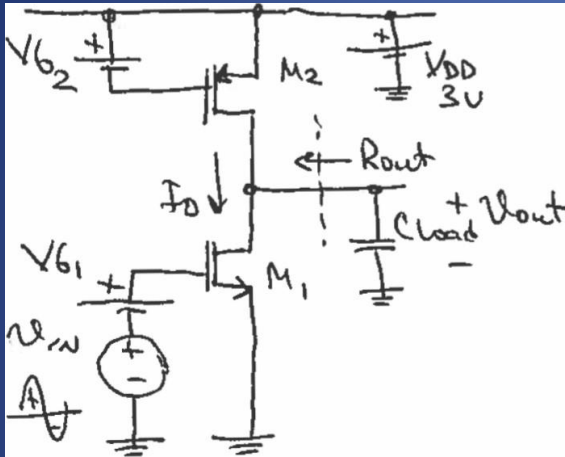
# Analysis of n-MOS common-source stage

$$(r_o = r_{on}) \Rightarrow (L_p = 2L_n)$$



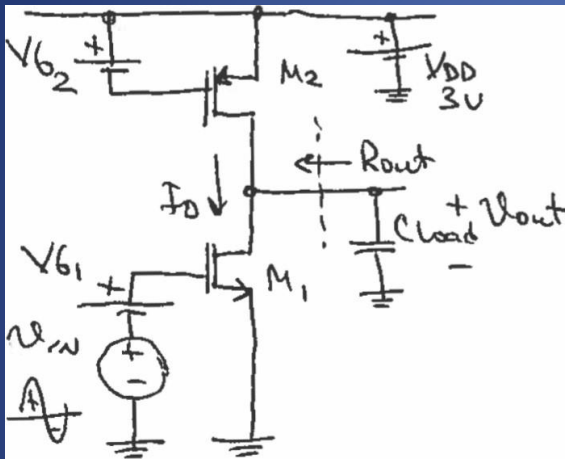
# nMOS common-source stage

$$(r_o = r_{on}) \Rightarrow (L_p = 2L_n)$$




# nMOS common-source stage

$$r_{op} = r_{on}$$

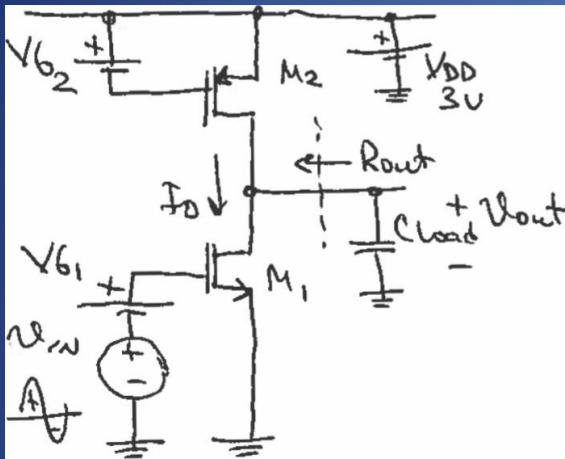


# nMOS common-source stage

$$L_p = 4L_n$$

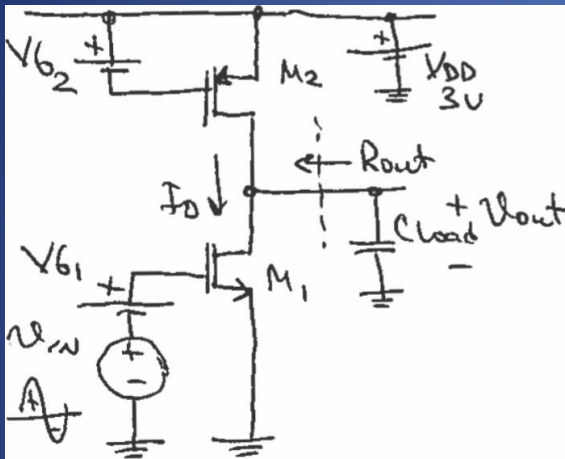

# nMOS common-source stage

$$L_p = L_n$$

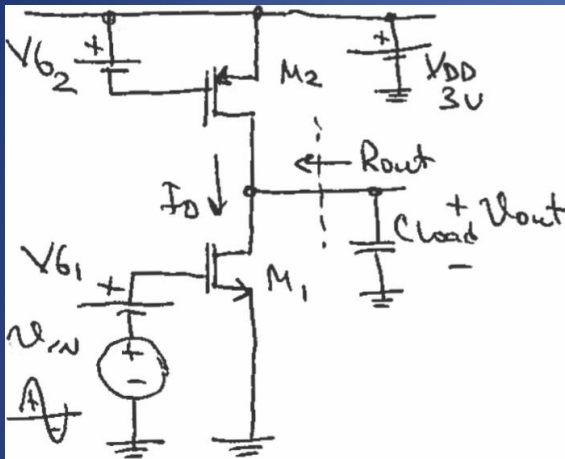




# Analysis of p-MOS common-source stage



# p-MOS common-source stage
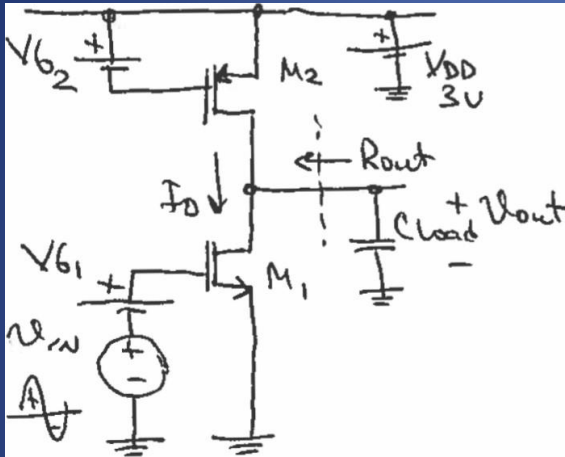
# Design of n-MOS common-source stage

$$(r_o = r_{on}) \Rightarrow (L_p = 2L_n)$$



# n-MOS common-source stage

$$(r_o = r_{on}) \Rightarrow (L_p = 2L_n)$$

