

## Homework 8

Common-source amplifier A and Cascode amplifier B operate on a 100 fF load capacitance  $C_1=C_2=C_{load}=100$  fF. Circuit B was obtained by incorporation of the common-gate stage M3 to circuit A.

All devices are biased to operate in the saturation region with the same transconductance  $g_m = 1$  mA/V. The MOSFET output resistances and  $C_{gs}$  and  $C_{gd}$  capacitances are as follows:

$r_{o_n} = r_{o1} = r_{o3} = 100$  kOhm,  $r_{o_p} = r_{o2} = 50$  kOhm

$C_{gs_n} = 20$  fF,  $C_{gs_p} = 60$  fF,  $C_{gd_n} = 5$  fF,  $C_{gd_p} = 15$  fF.

Consider a two-pole frequency response formed by two time constants:

- output resistance  $R_{out}$  seen by  $C_{load}$  and the total capacitive load  $C_{load} + C_{gd_n} + C_{gd_p}$ .
- input signal source resistance  $R_1=R_2=R_{sig}=100$  kOhm and the capacitance seen by  $R_{sig}$  at the gate of M1.

Note that in Amplifier B the Miller capacitance was reduced compared to that in Amplifier A due to reduction of the voltage gain of M1. Assignment:

- Calculate the DC voltage gain, the time constants forming two poles and the pole frequencies. Estimate the  $-3$ dB bandwidth for amplifiers A and B. Complete the table in the next page.
- Sketch the amplitude and phase responses of the voltage gain for amplifiers A and B on the provided Bode plot template. Note that inverting amplifiers have a 180 deg phase shift at low frequencies.

Upload a copy of page 2 to BSpace for grading.

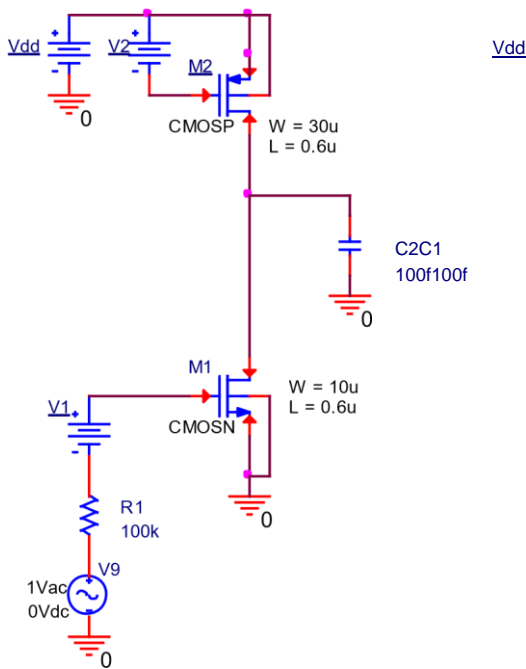


Figure A


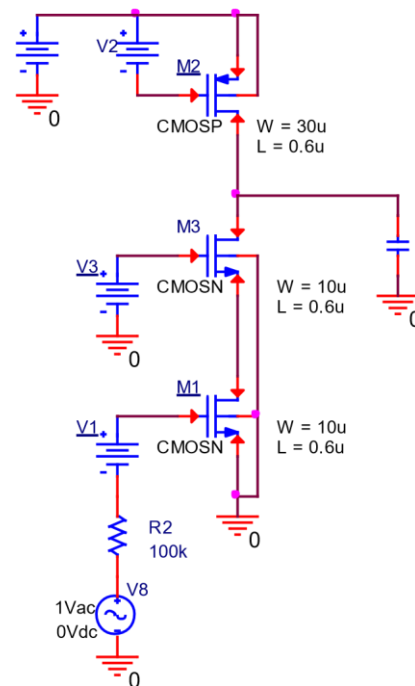



Figure B

Name \_\_\_\_\_ ID \_\_\_\_\_ Date \_\_\_\_\_

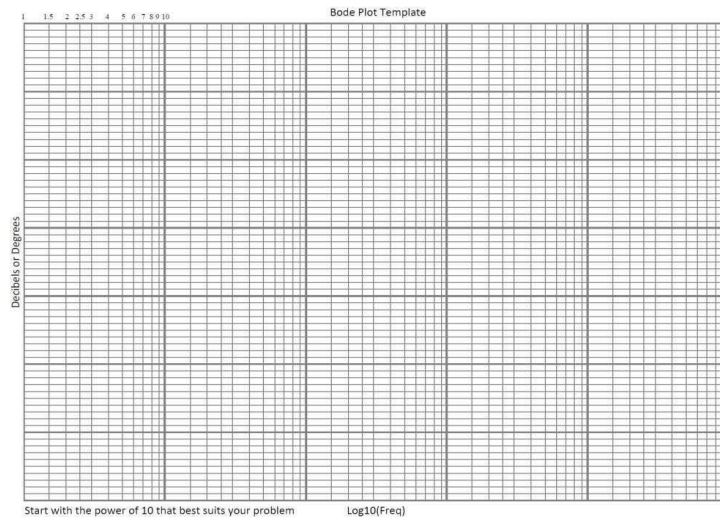1 . Amplitude responses of the voltage gain for amplifiers A and B.



Phase responses for amplifiers A and B.

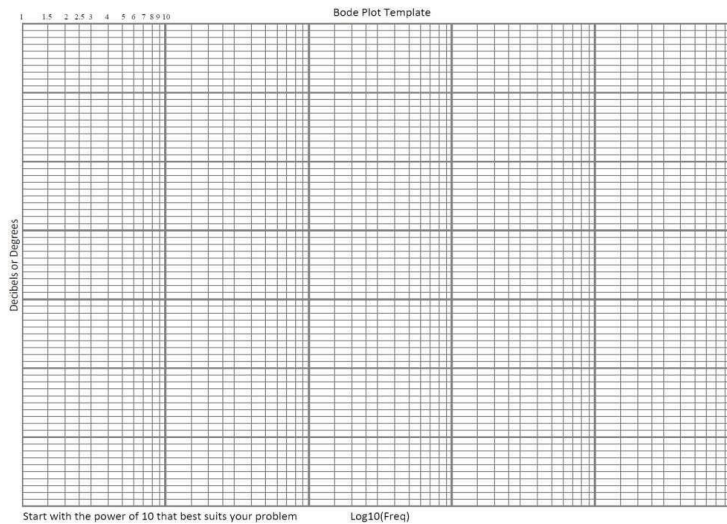

2. DC voltage gain, pole frequencies and bandwidth for the amplifiers

	A	B
DC voltage gain, dB		
1 <sup>st</sup> pole frequency (MHz)		
2 <sup>nd</sup> pole frequency (MHz)		
Bandwidth at -3 dB point (MHz)		